


# A TUTORIAL APPROACH TO ANALOG PHASE- LOCKED LOOPS

By Angsuman  
Roy

# PRESENTATION OUTLINE

- **Introduction and Terminology**
- **Analog PLLs**
- **Phase Detector (Mixer)**
- **Voltage-Controlled Oscillator**
- **Low-Pass Filter and Damping**
- **Applications**
  - **Frequency Synthesis**
  - **FM Demodulation**

# INTRODUCTION

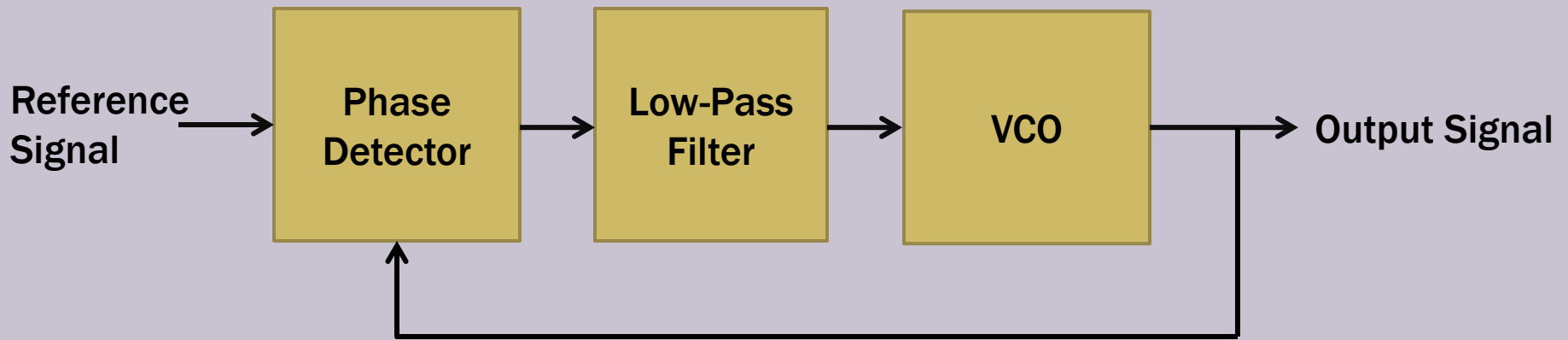

Basic Structure of a PLL

# TERMINOLOGY

## Analog PLL (APLL)

- Multiplying circuit (mixer) used for phase detector
- Other components are analog

## Digital PLL (DPLL)

- Mixer replaced with XOR gate or phase frequency detector (PFD)
- Other components are unchanged

## All Digital PLL (ADPLL)

- XOR Gate or PFD
- Other components are digital or numerically controlled.

# WHY ANALOG PLLS?


**Used for RF  
Circuits**

**Wide Tuning  
Range**

**Low Noise**

**Many  
Adjustable  
Parameters**


# APLL BLOCK DIAGRAM

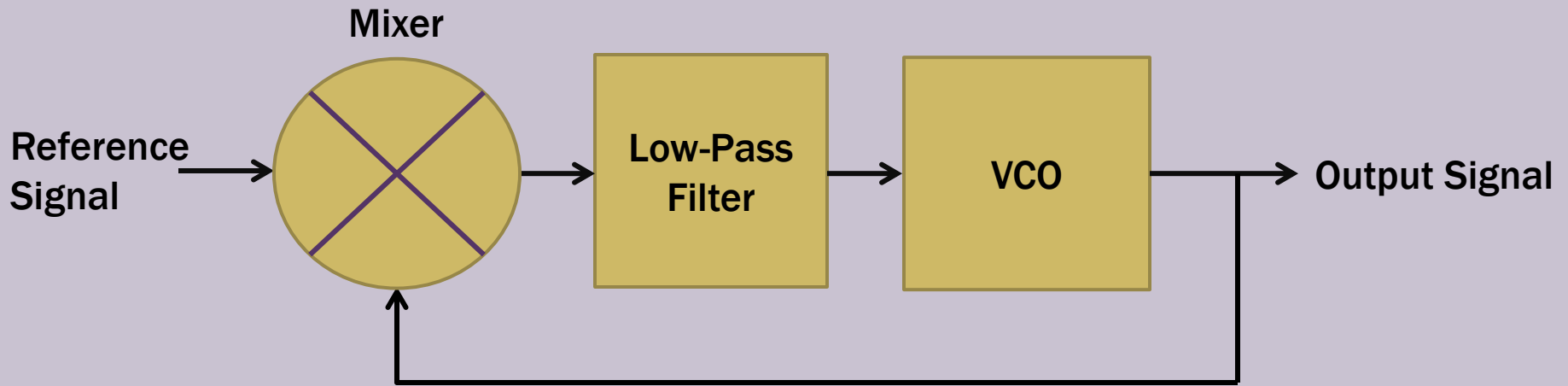

Basic Structure of a PLL
 
# WHAT IS A MIXER?

A mixer takes two input frequencies and outputs their sum and difference from the process of multiplication.



# MATH

$$V_1(t) = A_1 \cdot \sin(2\pi f_1 \cdot t)$$

$$V_2(t) = A_2 \cdot \sin(2\pi f_2 \cdot t)$$

$$V_1(t) \cdot V_2(t) = \sin(2\pi f_1 \cdot t) \cdot \sin(2\pi f_2 \cdot t)$$

$$\text{Trigonometric Identity: } \sin(a) \cdot \sin(b) = \frac{1}{2} [\cos(a - b) - \cos(a + b)]$$


$$V_1(t) \cdot V_2(t) = \frac{1}{2} (A_1 \cdot A_2) \cdot [\cos(2\pi(f_1 - f_2)t) - \cos(2\pi(f_1 + f_2)t)]$$

  
Difference


  
Sum



# CONCEPTUAL DIAGRAM

 


# MIXER DESIGN: 4 QUADRANT MULTIPLIER

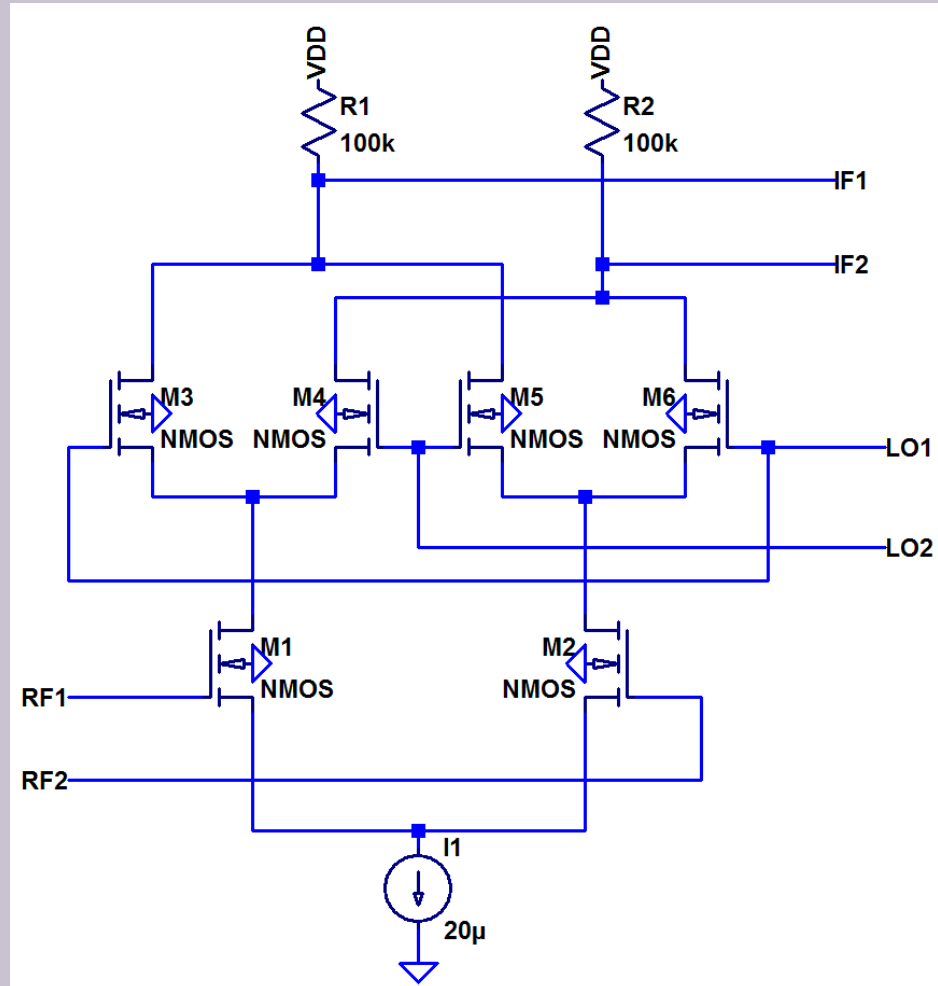

# 4 QUADRANT MULTIPLIER DEVICE SIZES

1.8u/0.6u  
min size devices


for speed

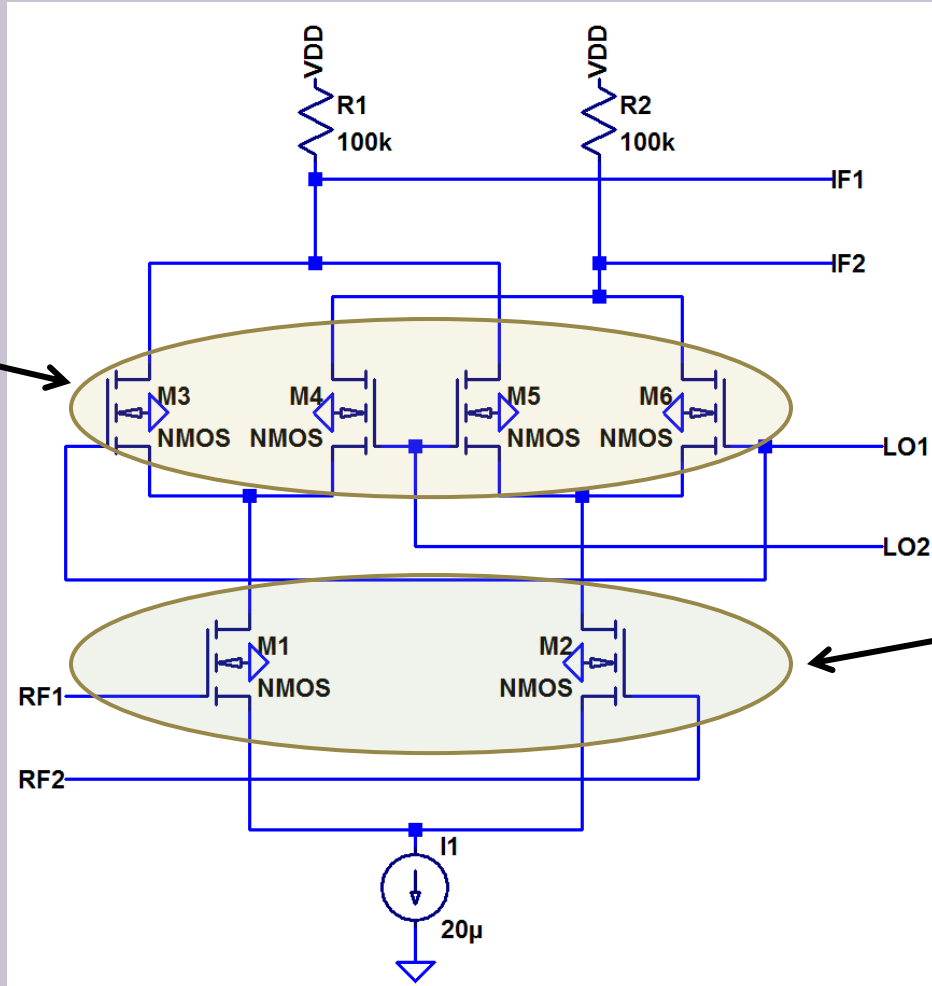


6u/0.6u for current  
sinking ability
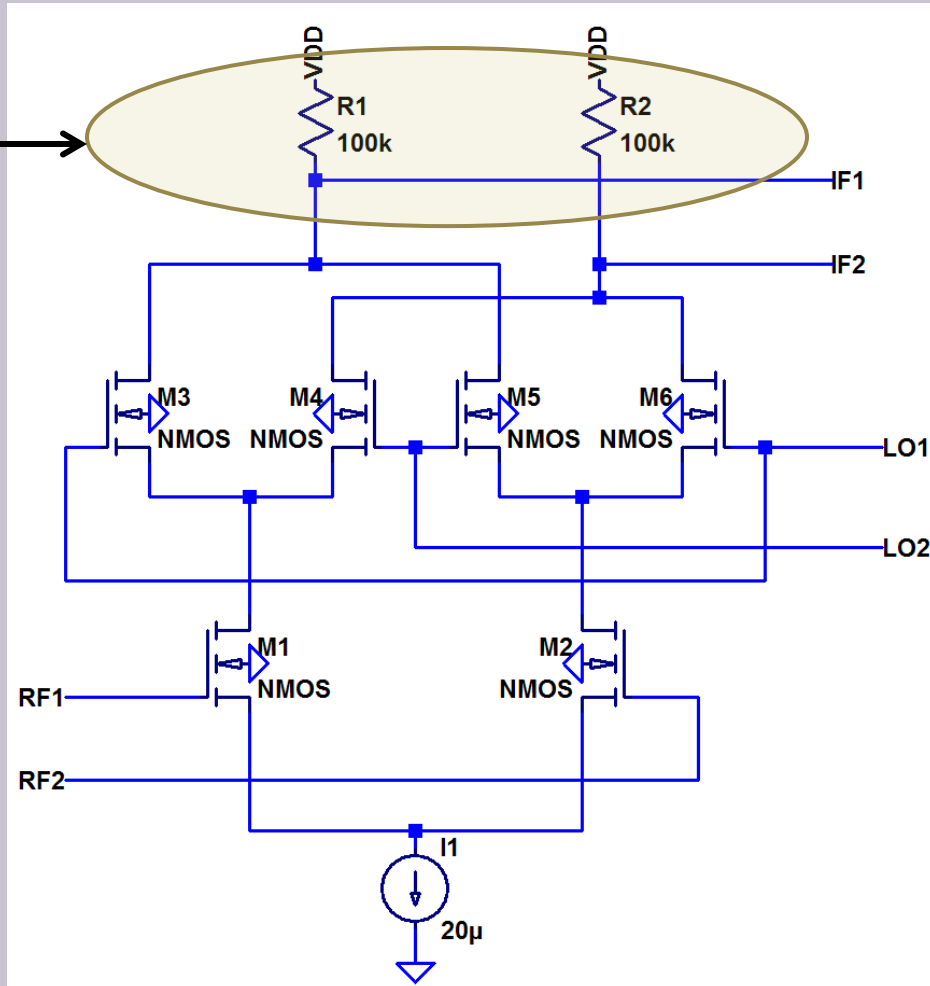
# 4 QUADRANT MULTIPLIER GAIN

Output voltage is developed across these resistors




# AC OPERATION OF THE MIXER

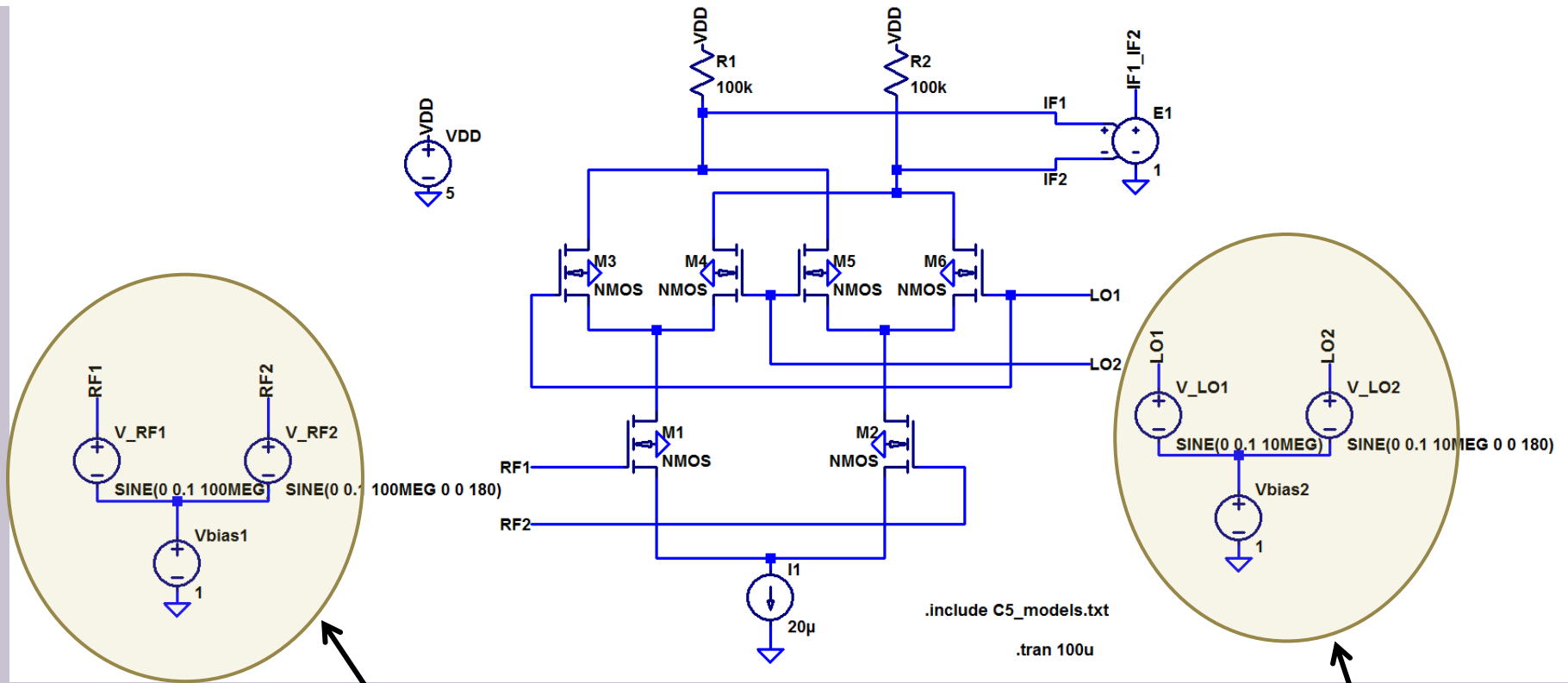

Differential sine input with bias voltage represents RF input of 100 MHz

Same, but LO input of 10 MHz


# TIME DOMAIN VIEW OF INPUTS/OUTPUT

 


# FFT OF IF OUTPUT

Difference frequency: 90 MHz

Sum frequency: 110 MHz

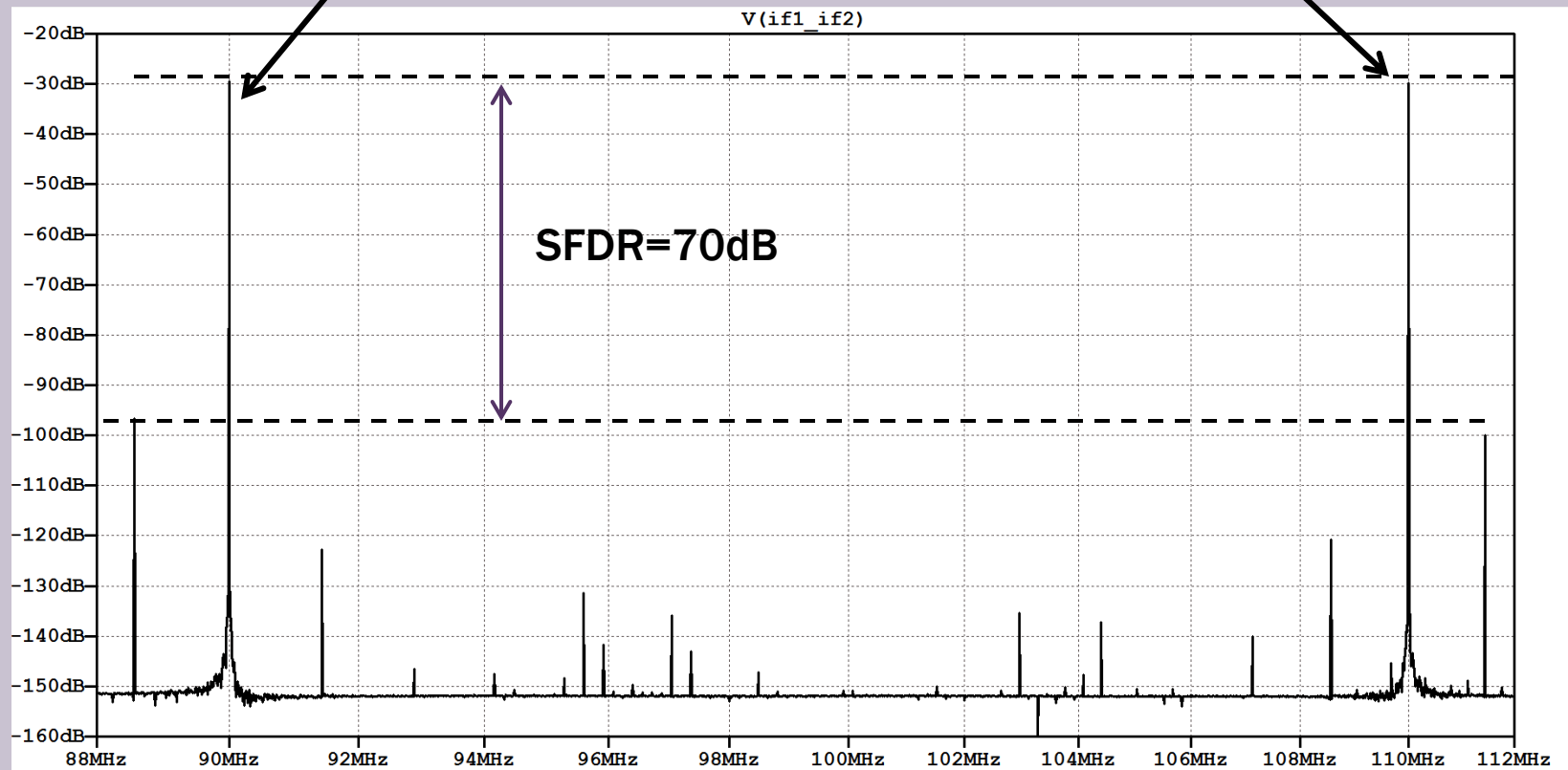


# GAIN AND NOISE

 




# 4 QUADRANT MULTIPLIER GAIN

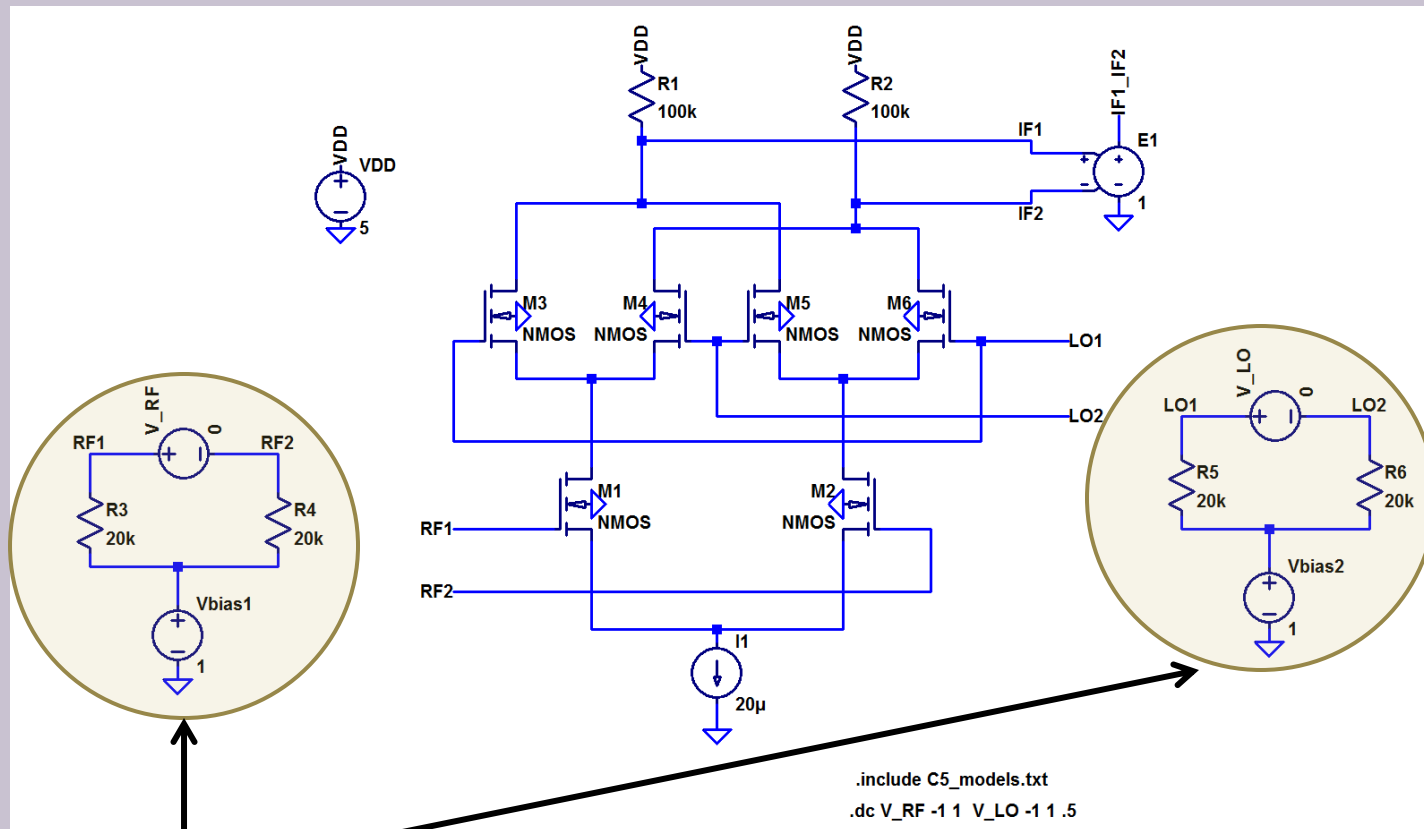

Network to allow for sweeping differential voltages while keeping a fixed bias.

`.dc V_RF -1 1 V_LO -1 1 0.5`


# 4 QUADRANT MULTIPLIER GAIN

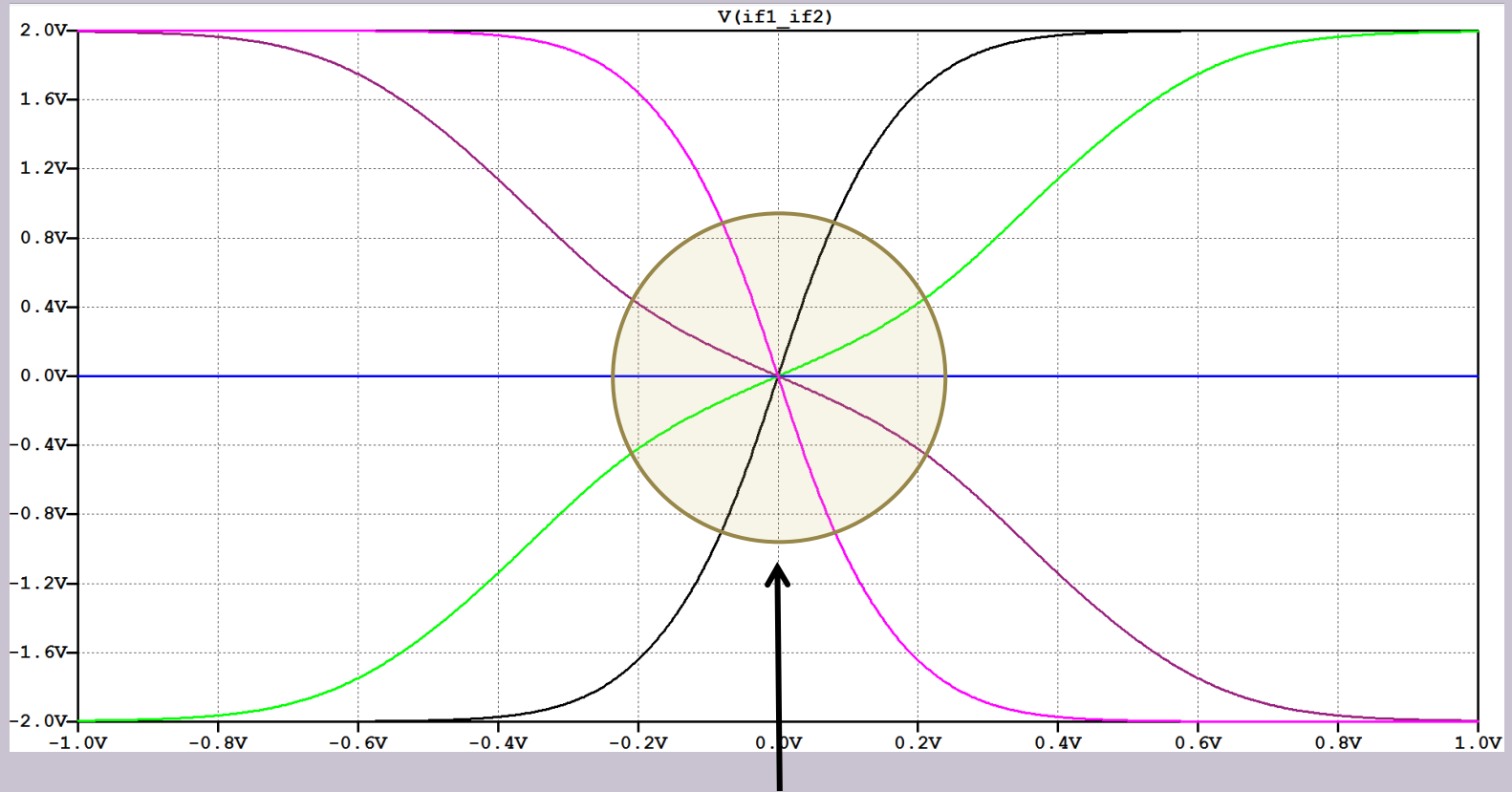


Linear only for small signals
 
# 4 QUADRANT MULTIPLIER GAIN

Changed sweep and step settings to show linear region better



# LET'S MULTIPLY

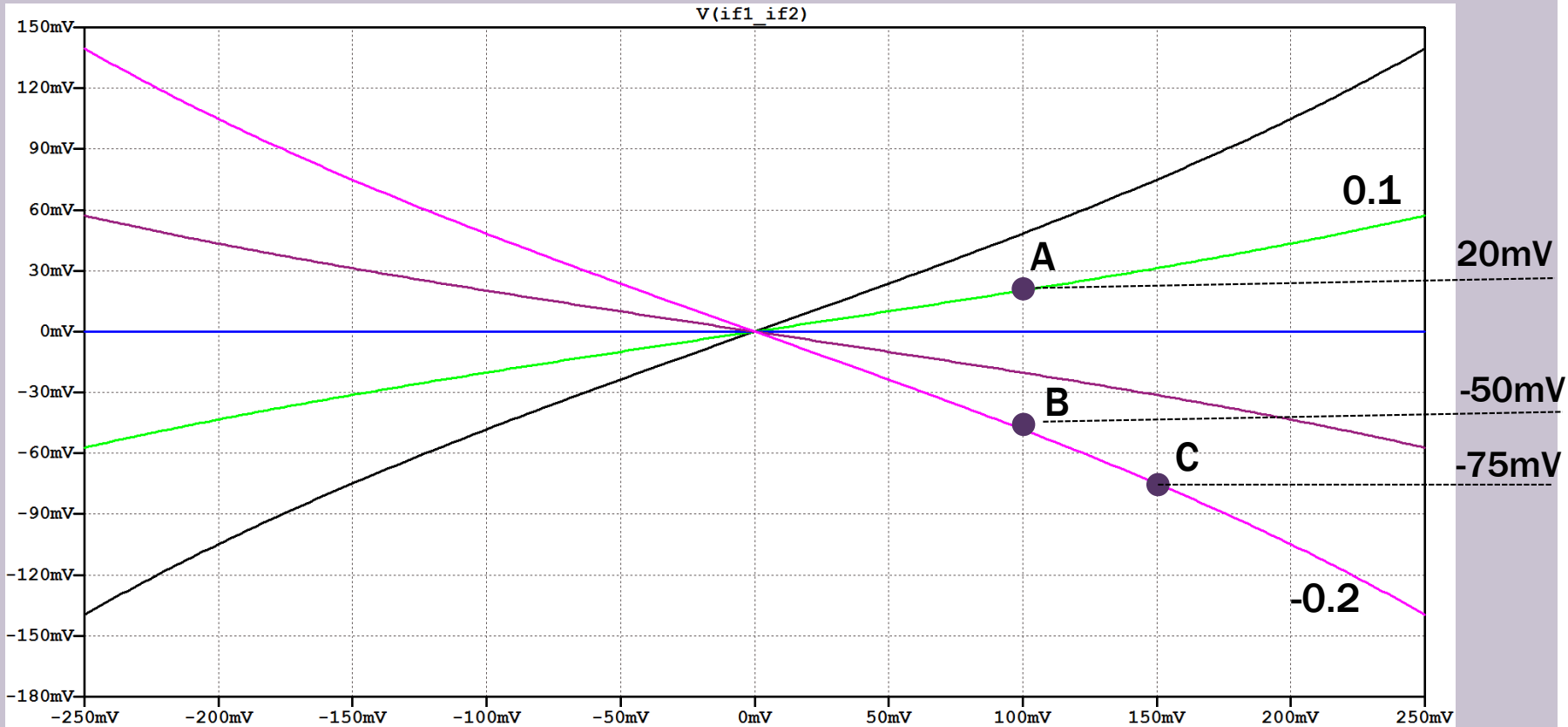


Point A:  $K \cdot (0.1V \cdot 0.1V) = 0.02V \rightarrow K=2$

Point A:  $K \cdot (0.1V \cdot -0.2V) = -0.05V \rightarrow K=2.5$

Point C:  $K \cdot (0.15V \cdot -0.2V) = -0.075V \rightarrow K=2.5$

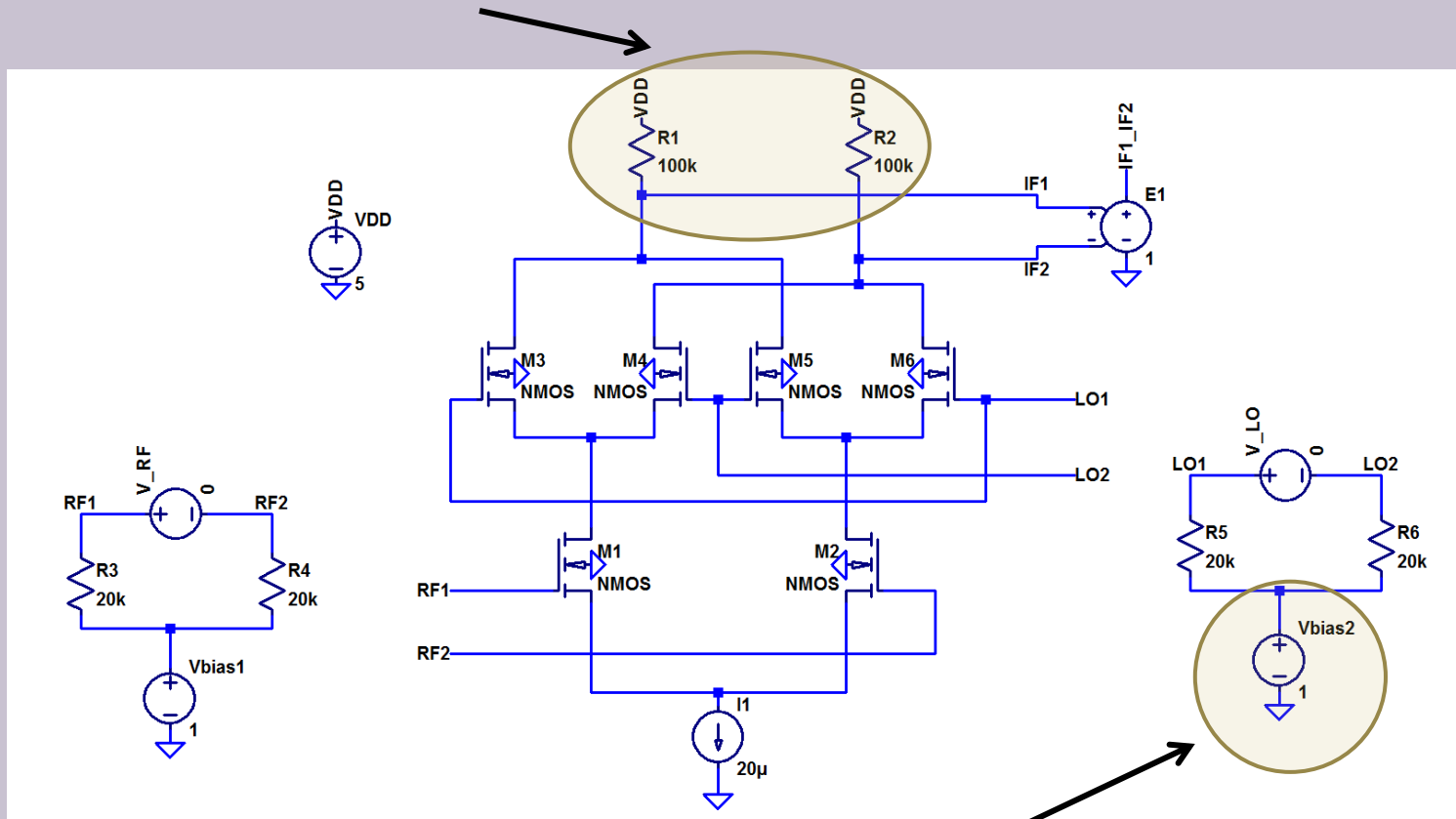
# INCREASING GAIN

Increasing the value of these resistors increases gain but reduces load driving ability.




Increasing the bias voltage increases gain and allows for variable gain.

# REPLACING RESISTORS

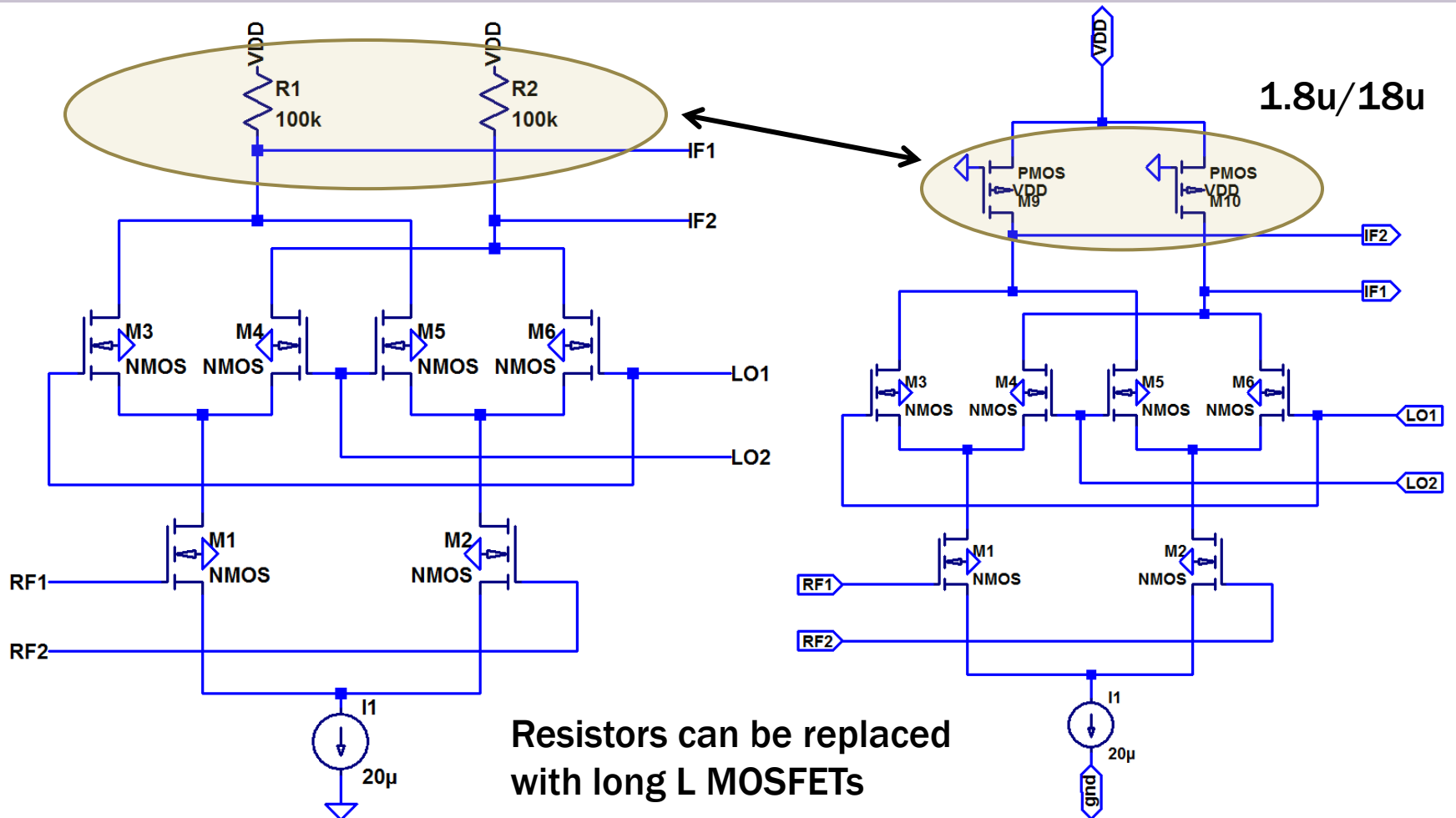
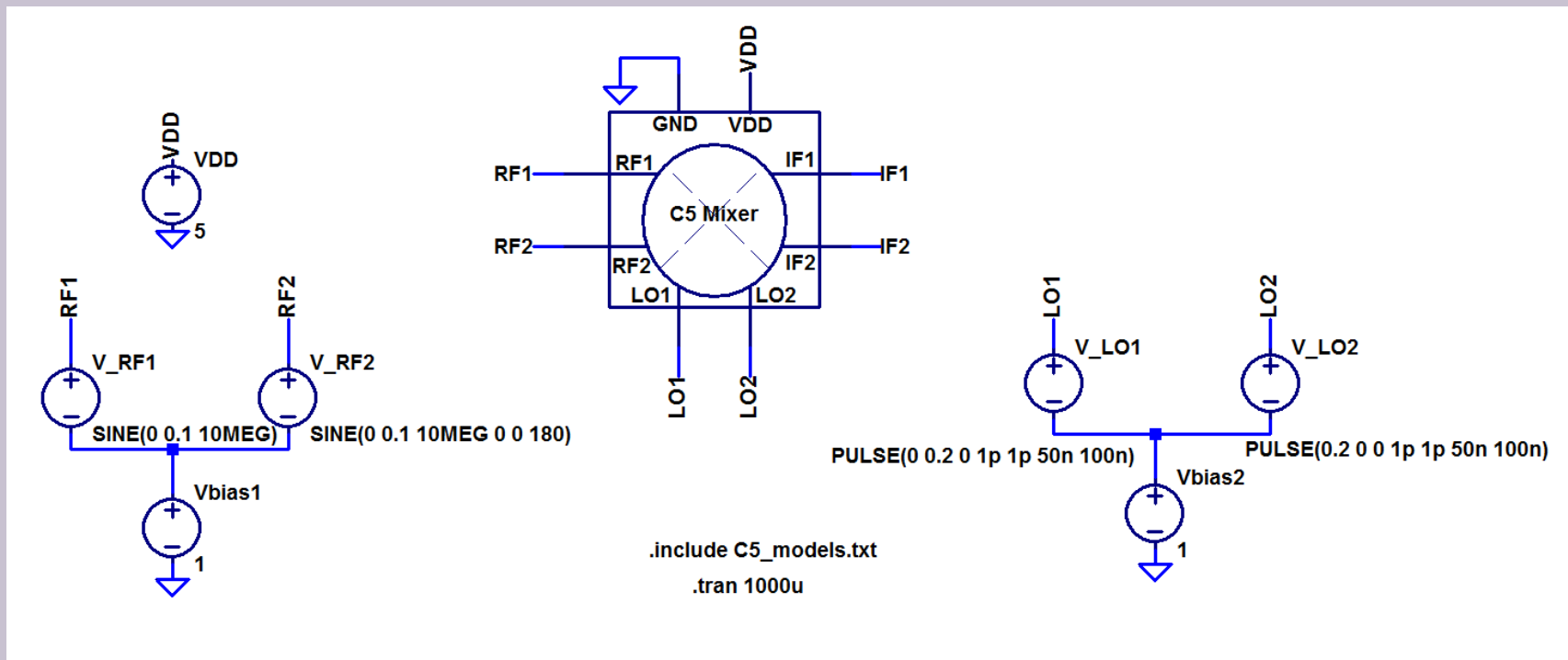
# MIXER AS PHASE DETECTOR


When both RF and LO frequencies are the same, the mixer operates as a phase detector.



Simulation test set-up
 
# NO PHASE DIFFERENCE


IF output is rectified at twice the RF/LO frequency.  
Averaging this will result in some DC value.




 
# 90 DEGREE PHASE DIFFERENCE

IF output appears to have zero average value.




IF

LO

RF


There is a relationship between average IF voltage and phase between LO and RF.

# FILTERING THE IF OUTPUT

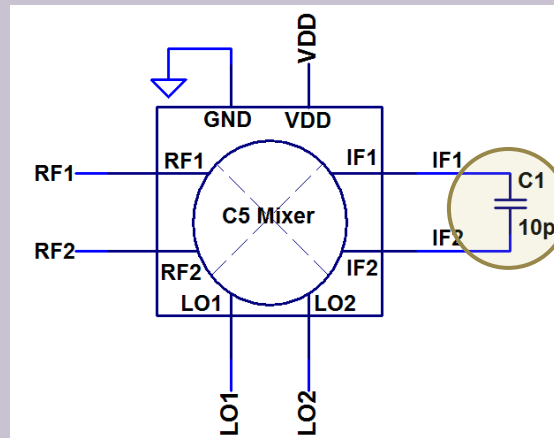


Capacitor to filter IF output

IF output is now a DC value

 


# IF OUTPUT AS A FUNCTION OF PHASE

 

# ZOOMED IN

## Output Voltage as a Function of Phase

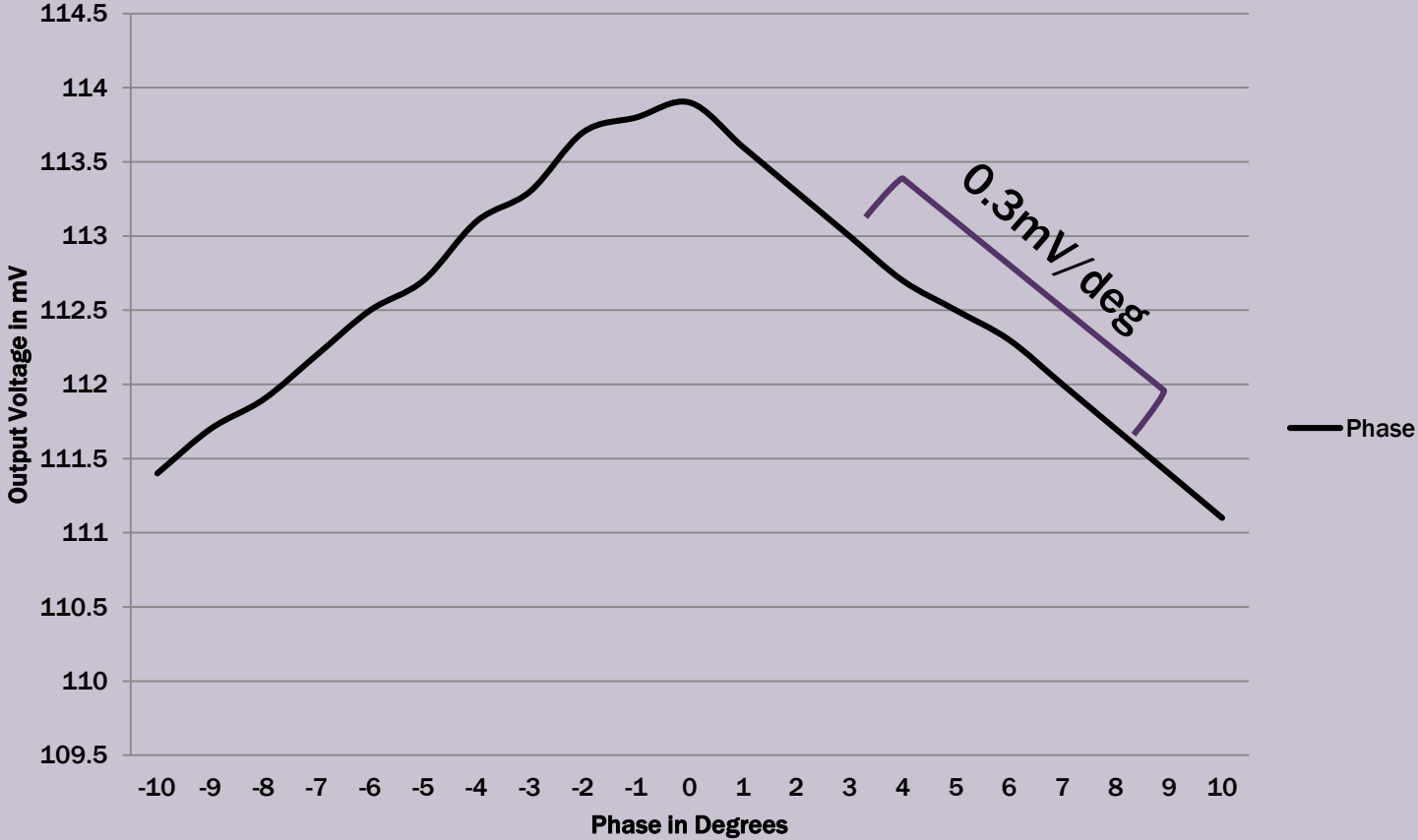


# VCO DESIGN

- **Many options to choose from**
  - Ring oscillators
  - Relaxation oscillators
  - Varactor-tuned LC oscillators
- **Requirements are**
  - Relatively linear
  - Has the tuning range needed for the intended application
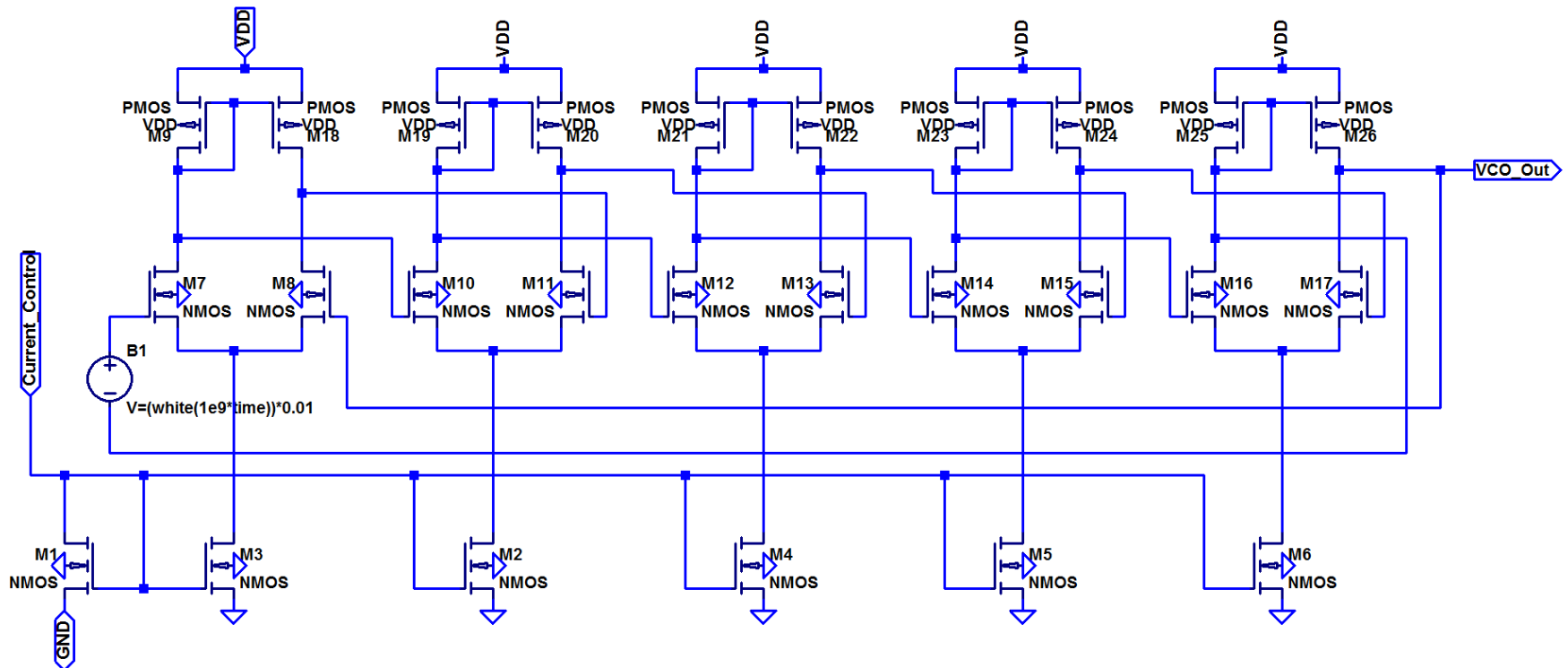
# DIFFERENTIAL RING OSCILLATOR

Same idea as a ring oscillator made from inverters but with differential amplifiers.




# BREAKING IT DOWN

Current mirror loads (3.6u/0.6u)

Current sets delay

Output

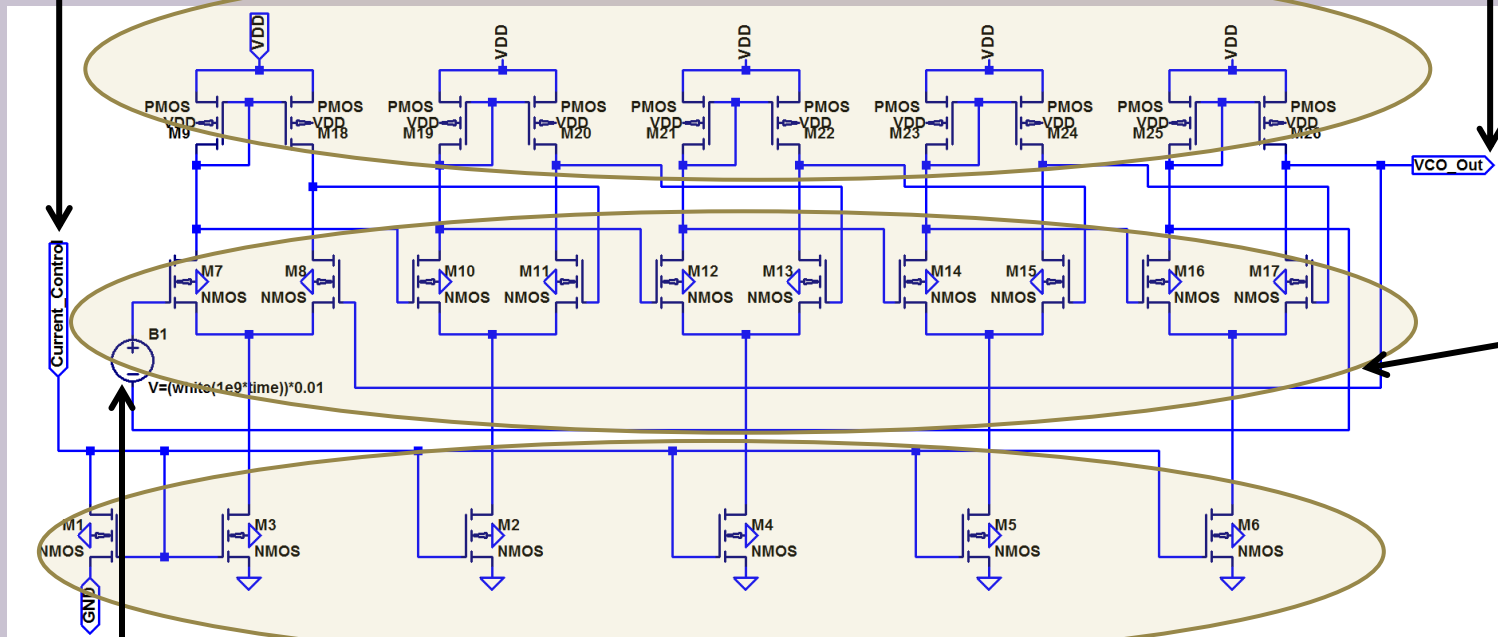


Diff pairs (1.8u/0.6u)

White noise source for simulation

Current mirrors (3.6u/0.6u)

# OUTPUT

**Problem: Odd output waveform shape**

 

**Problem: Output does not swing to full logic levels**

## Solution


**Level Shifting** Need to shift the center of the output to  $\frac{1}{2}$  VDD so inverters switch in the middle of the waveform.

**Pulse Shaping** Inverter string is needed to provide full logic levels and sharpen the pulses.




# LEVEL-SHIFTING

Level shifter with long L MOSFETs

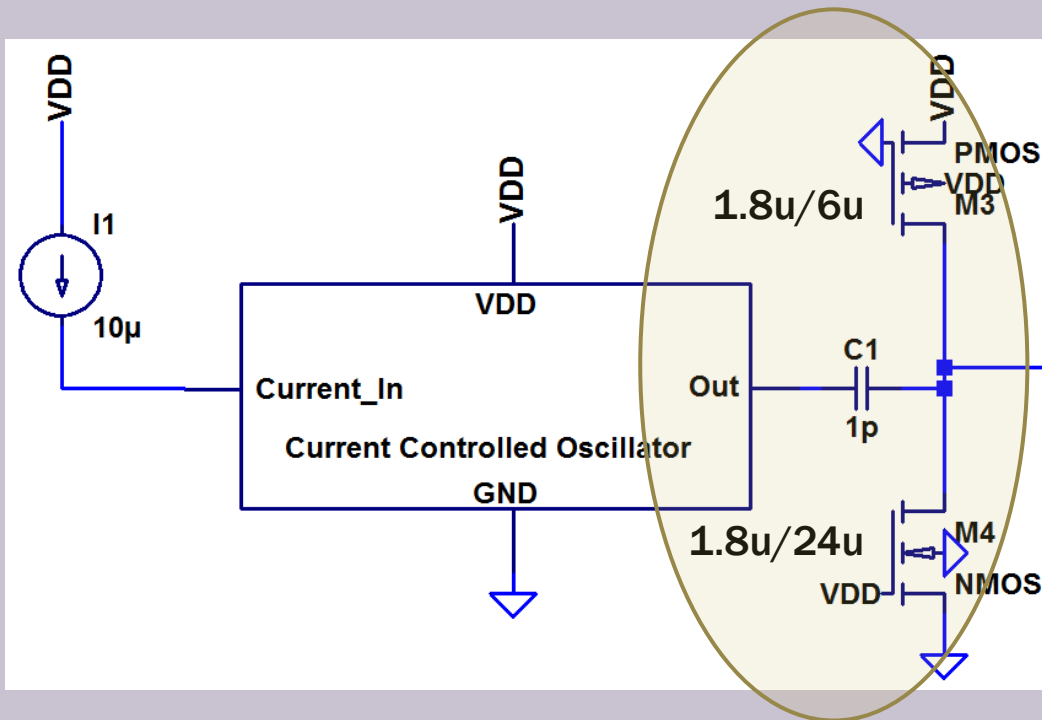


Can also use resistors

 

# INVERTER STRING

Small inverter for low capacitive loading

Big inverter for load driving ability

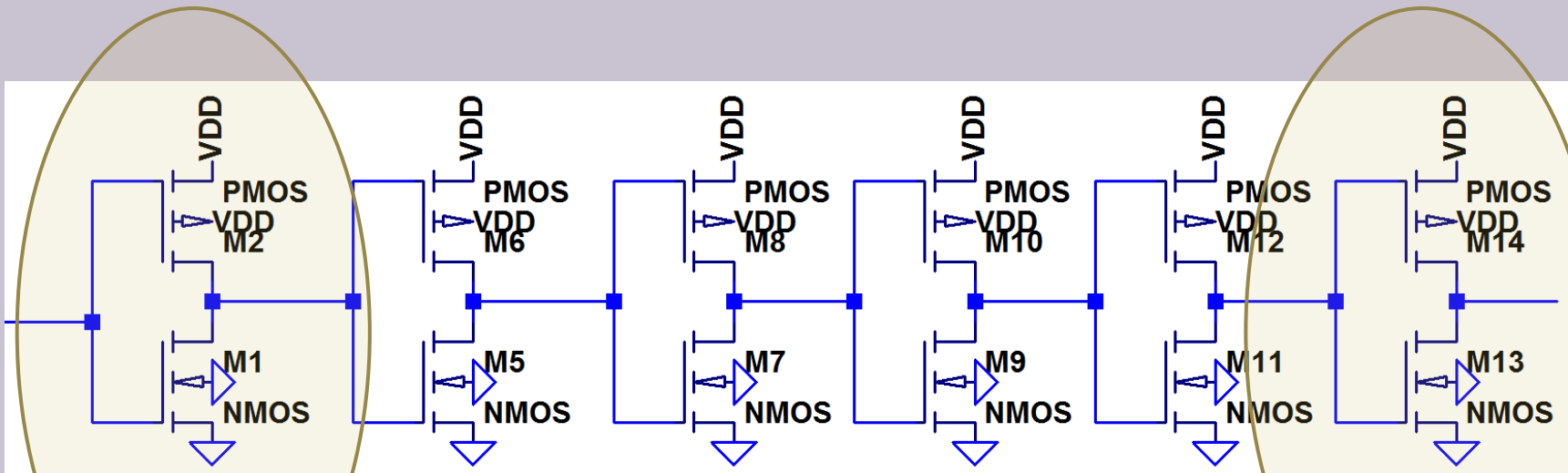

6/3

6/3

6/3

12/6


24/12

48/24

Inverter sizes are  
PMOS Width/NMOS Width

# RESULT


300 MHz

 


Sharp transitions with 50% duty cycle

# FREQUENCY TESTING

## Frequency as a Function of Current

 


# VOLTAGE TO CURRENT CONVERTER

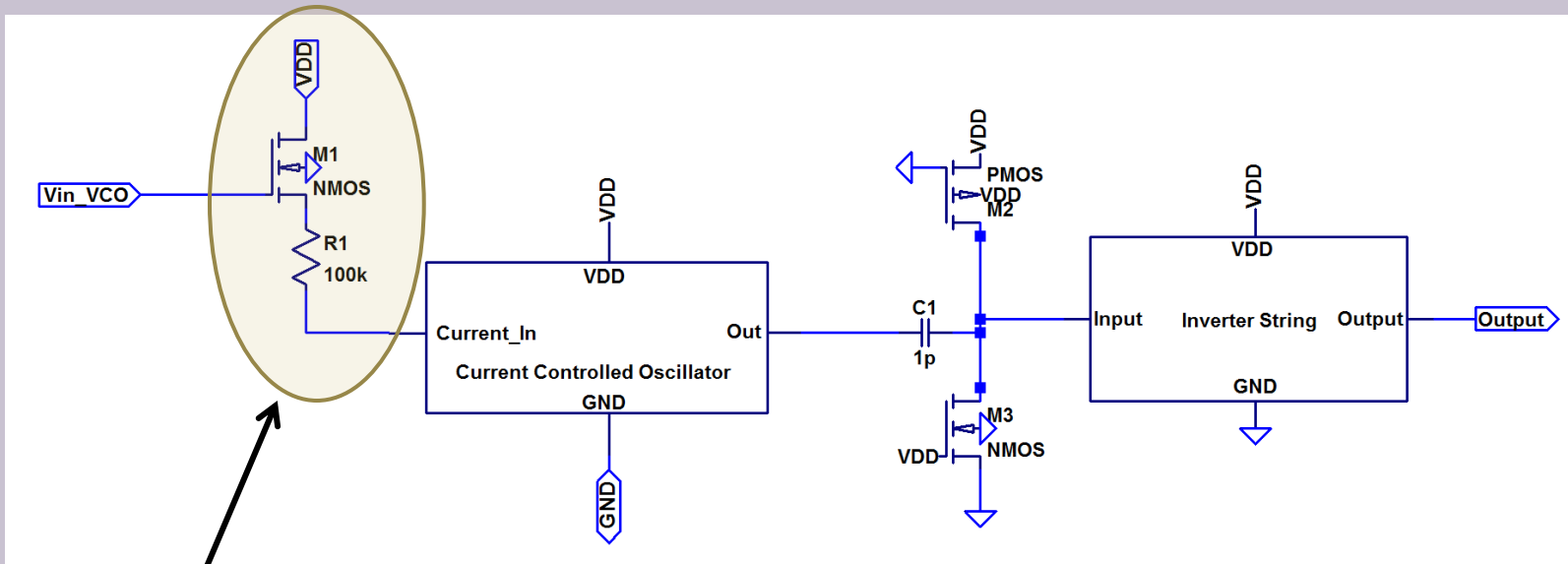

This MOSFET and resistor serves as a rudimentary voltage to current converter.

# FREQUENCY TESTING


## Frequency as a Function of Voltage

 
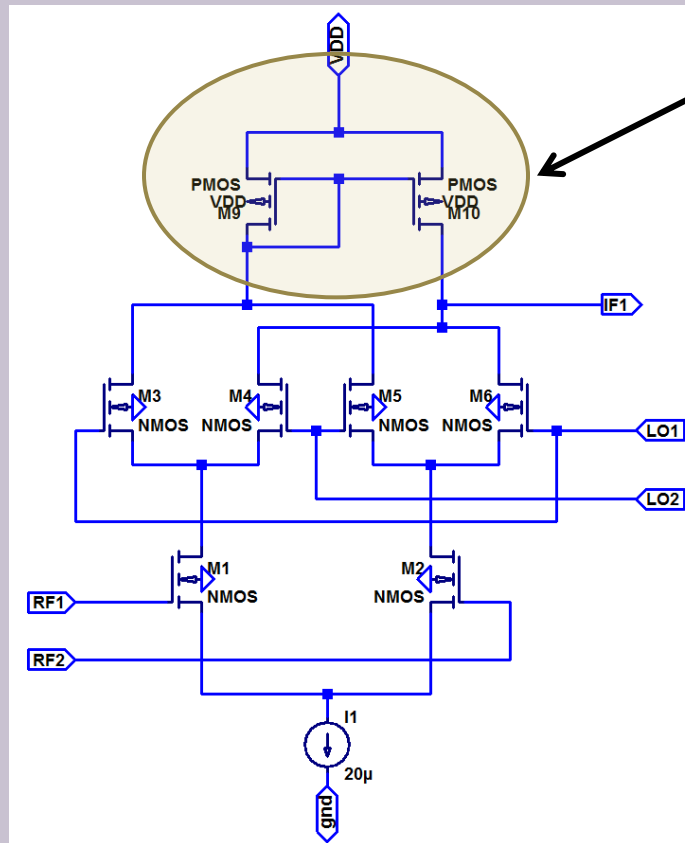
# INTERFACING MIXER TO VCO

Mixer output is differential while VCO input is single-ended.


Active load for differential to single ended conversion.



Single ended mixer
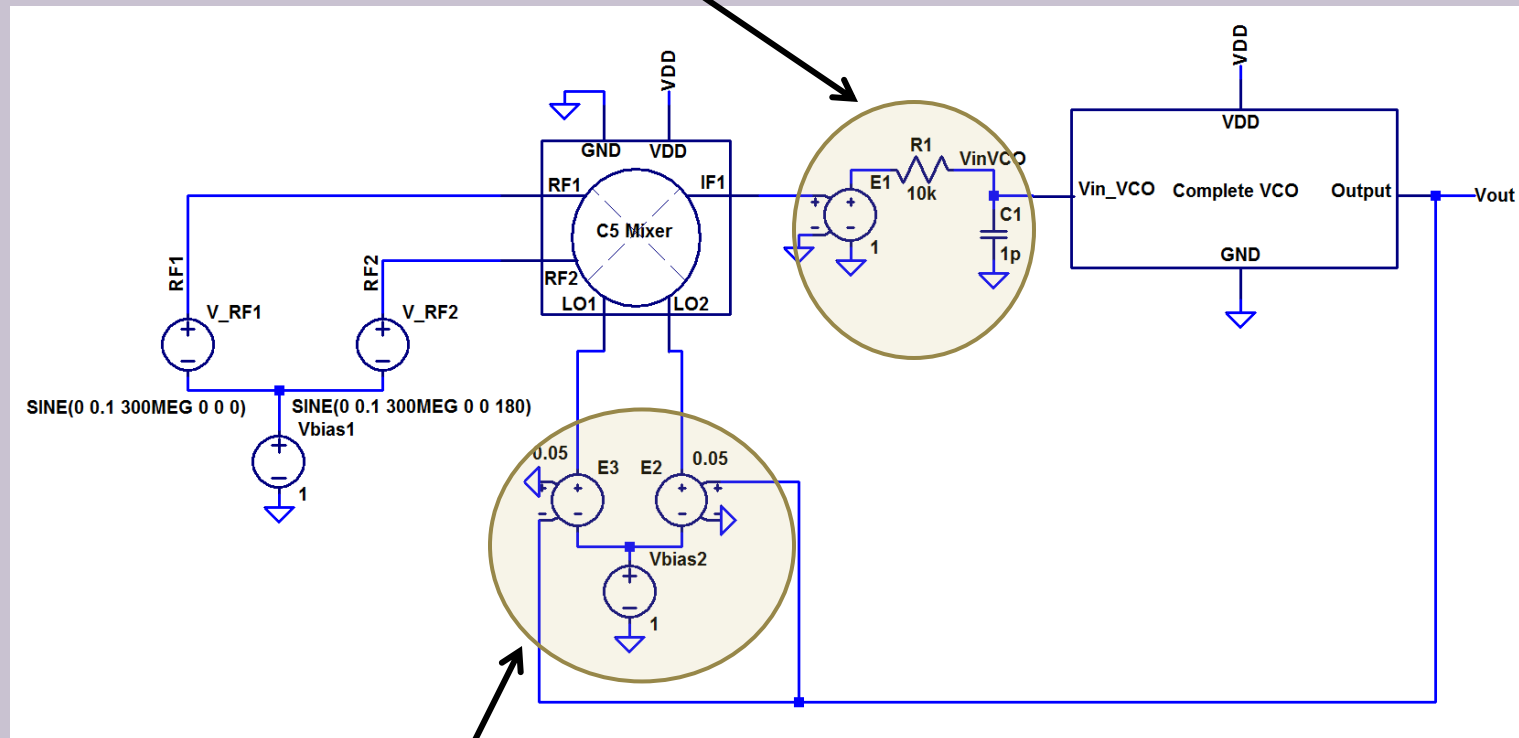
# CLOSING THE LOOP


Loop filter with buffer to isolate effects from mixer output impedance.



Mixer needs proper biasing and input levels.



# OUTPUT

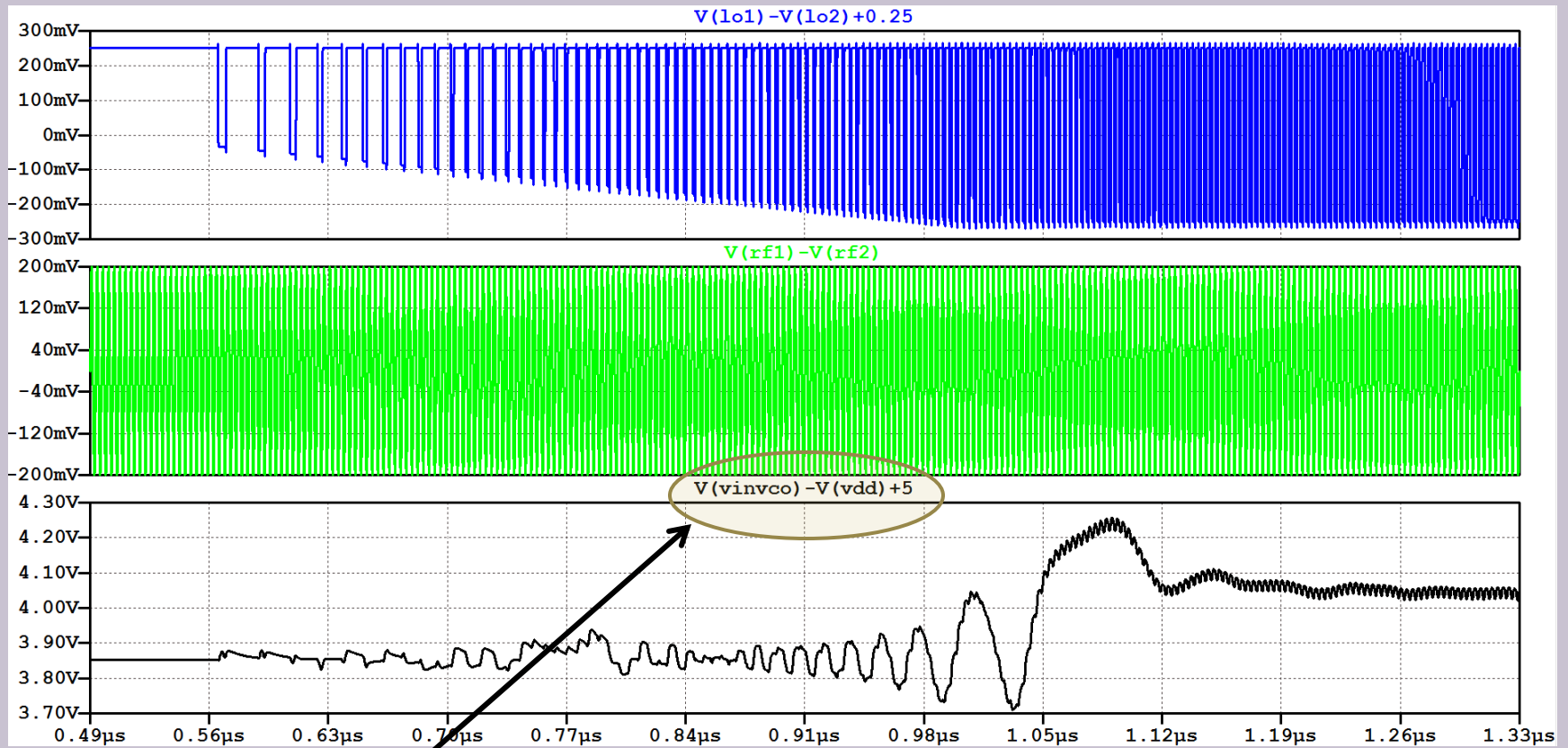


LO

RF

Vin  
VCO

Isolating start-up transients

# LOCKED OUTPUT AT 300 MHz

 

Edges line up

# USEFUL EQUATIONS

$$K_F = \frac{1}{1 + sRC} \quad \left. \vphantom{K_F} \right\} \text{Loop filter transfer function (simple 1}^{\text{st}} \text{ order lowpass)}$$


$$H(s) = \frac{\varphi_{LO}}{\varphi_{RF}} = \frac{K_{PD}K_{VCO} \cdot \frac{1}{1 + sRC}}{s + \frac{1}{N}K_{PD}K_{VCO} \cdot \frac{1}{1 + sRC}} \quad \left. \vphantom{H(s)} \right\} \text{System transfer function (2}^{\text{nd}} \text{ order)}$$

$$\omega_n = \sqrt{\frac{K_{PD}K_{VCO}}{N \cdot RC}} \quad \left. \vphantom{\omega_n} \right\} \text{Natural frequency}$$

$$\zeta = \frac{1}{2RC\omega_n} \quad \left. \vphantom{\zeta} \right\} \text{Damping ratio}$$

**N is for the divider ratio in frequency synthesis examples. If there is no divider use N=1.**


# OVERDAMPED CASE

 


Overdamped PLL not locking on a single frequency

FFT of output shows two peaks at 300 MHz and a noisy one at 291 MHz.

The difference is the natural frequency.

 


# UNDERDAMPED CASE

 


**VinVCO voltage shows some oscillation and ripple voltage.**

**FFT of output shows the correct peak at 300 MHz but there is significant phase noise.**

# CRITICALLY DAMPED CASE

 

 **VinVCO voltage settles and looks fairly random.**





**FFT of output shows the correct peak at 300 MHz with less noise.**

# APPLICATION: FREQUENCY SYNTHESIS

- **Stable oscillator topologies don't scale well to high frequencies.**
  - Quartz (32 KHz-160 MHz)
  - Rubidium (typically 10 MHz)
  - Silicon MEMS (1 MHz-140 MHz)
- **A PLL locked to a stable reference can generate a stable high frequency oscillator.**
  - Quartz (10 PPM)
  - Silicon MEMS (100 PPM)
  - Rubidium (0.0001 PPM or 0.1 PPB)


# FREQUENCY DIVIDER

Each stage divides by 2

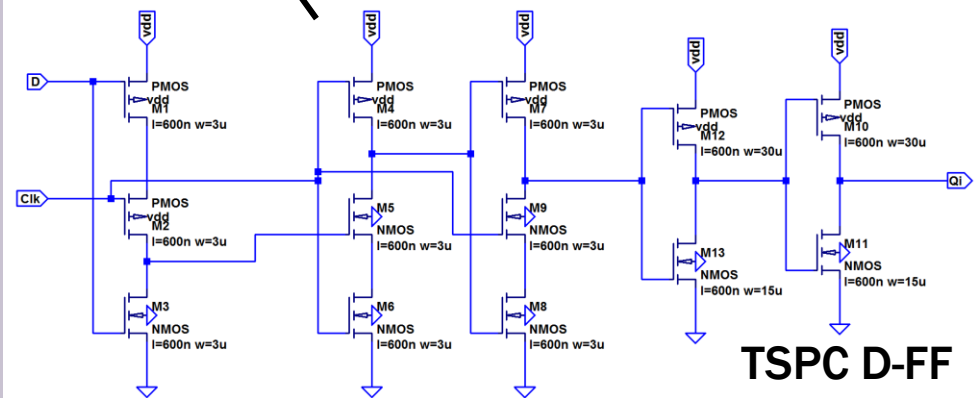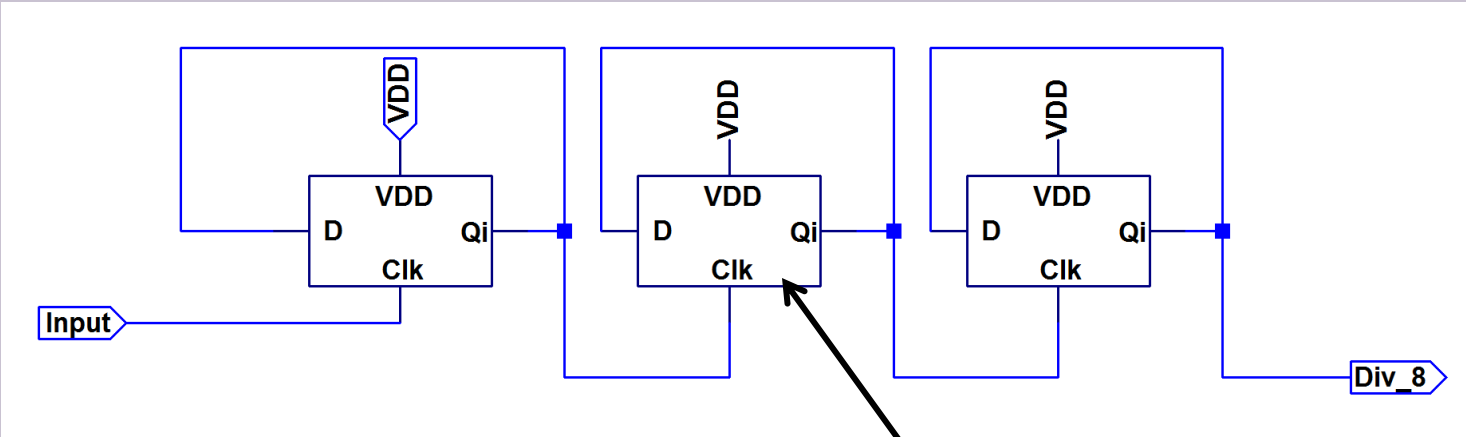




# FREQUENCY MULTIPLIER SCHEMATIC

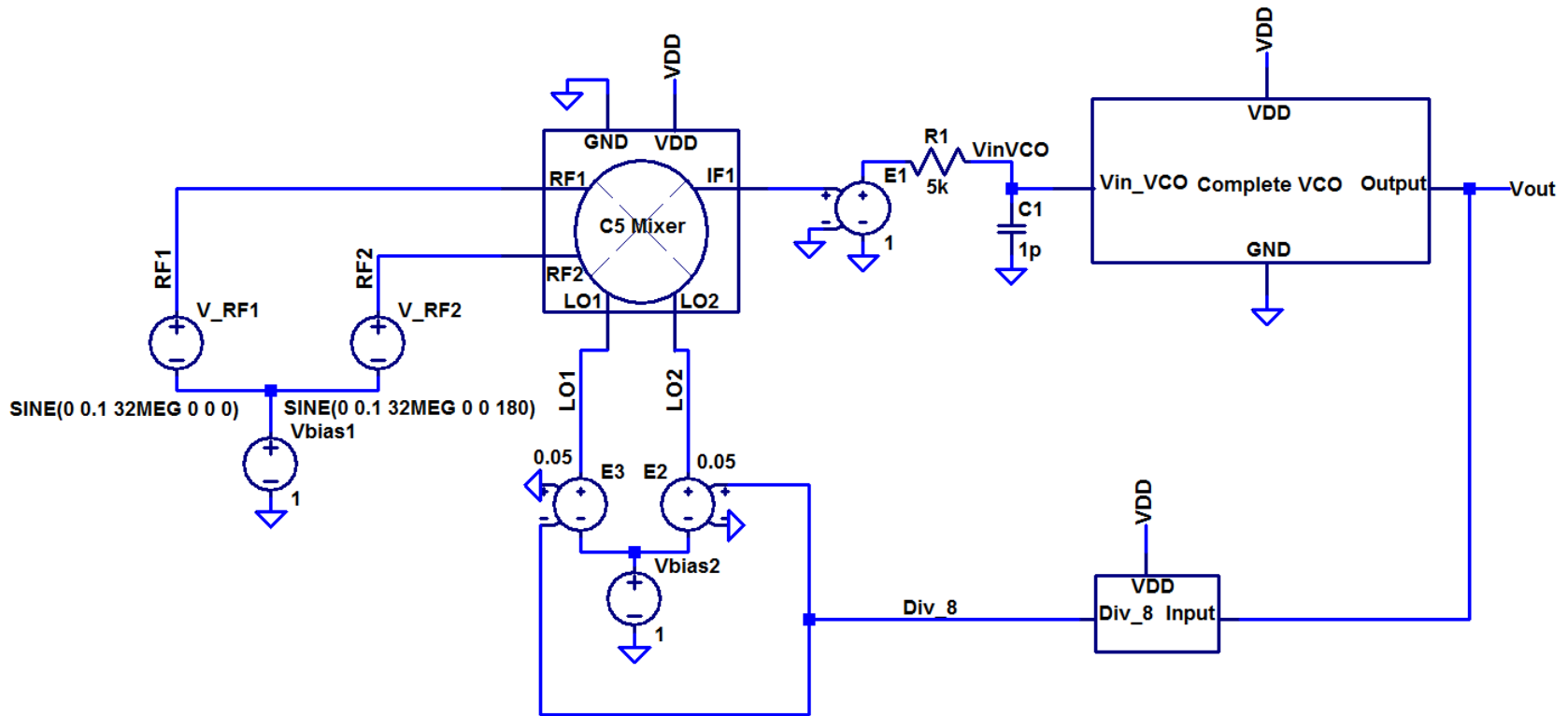


# OUTPUT

## 256 MHz Output

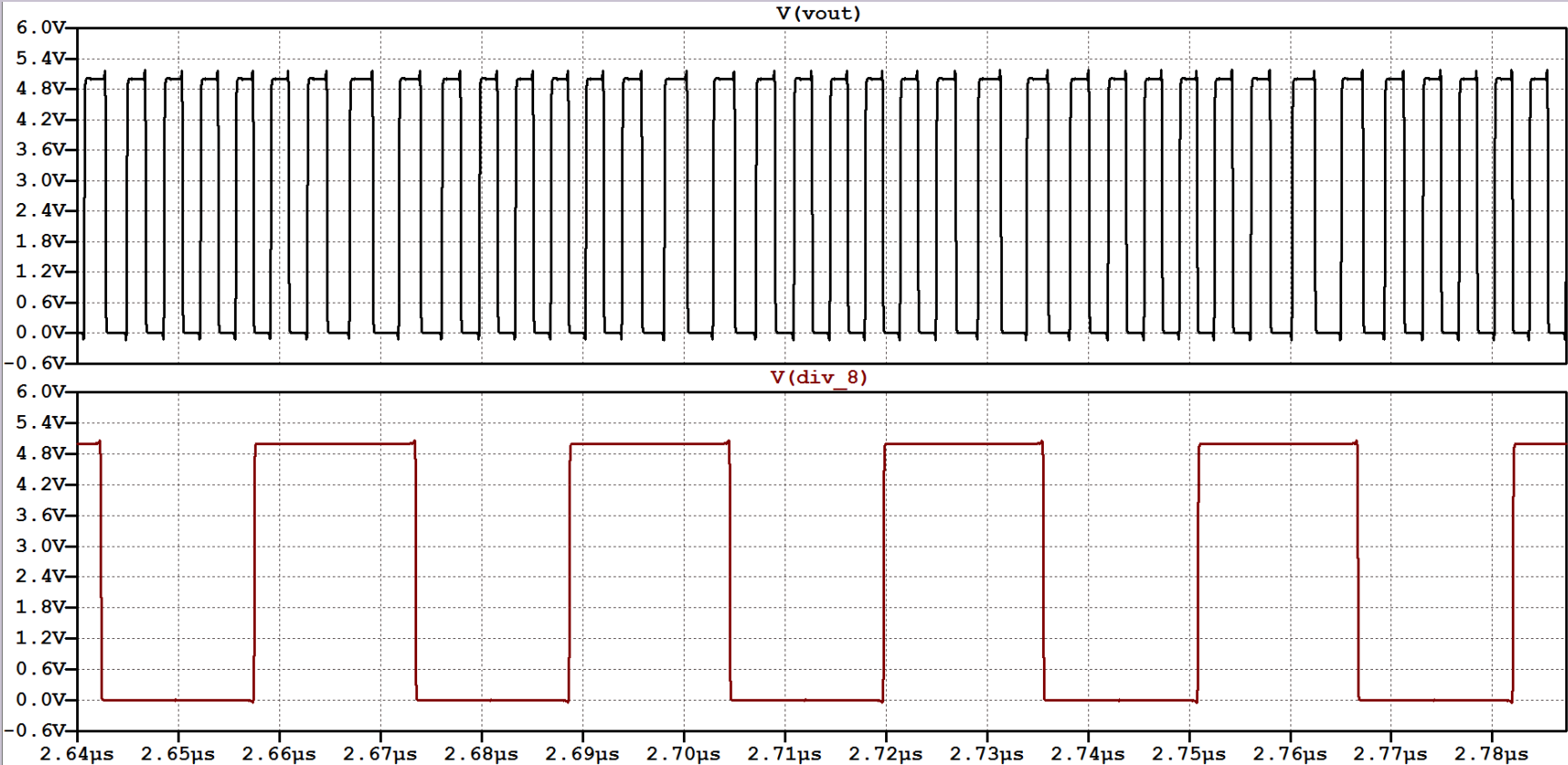

## 32 MHz Input

# APPLICATIONS: FM DEMODULATION

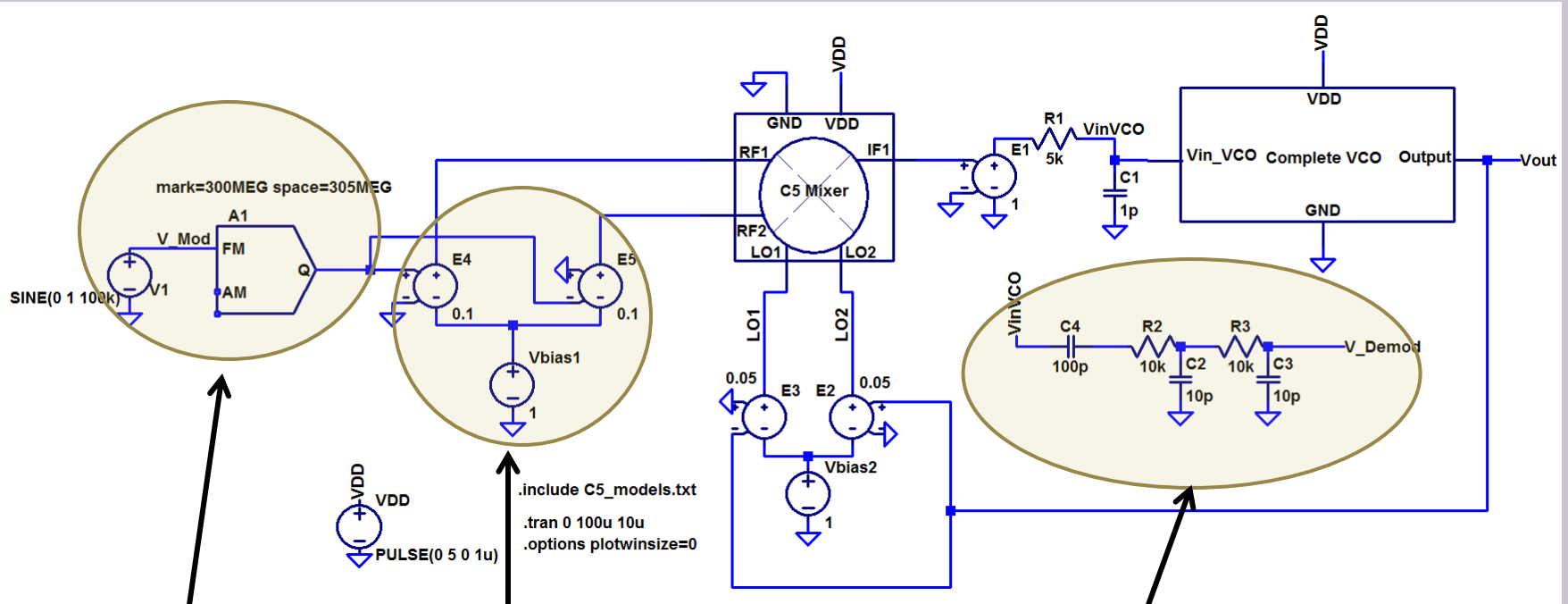


FM Modulator

Provides differential input at correct amplitude

Additional filtering to filter out VCO ripple

# INPUTS AND OUTPUTS

 


Filtered  
VCO  
input

VCO input

Original  
signal

# APPLICATIONS: FSK DEMODULATION

 

Filtered  
VCO  
input

VCO input

Original  
Input to  
FSK  
Modulator

# REFERENCES

- *The Art of Electronics* by Horowitz and Hill
- MT-080 Mixers and Modulators by Analog Devices
- MT-086 Fundamentals of PLLs by Analog Devices
- Practical Tips for PLL Design by Dennis Fischette
- FM & PM Demodulation from *The Scot's Guide to Electronics*
- Mixer Basics Primer by Christopher Marki