

EE320L Electronics I

Laboratory

Laboratory Exercise #10

Frequency Response of BJT Amplifiers

By

Angsuman Roy

Department of Electrical and Computer Engineering

University of Nevada, Las Vegas

Objective:

The purpose of this lab is to understand the parameters that affect the frequency response of a BJT amplifier and apply this knowledge to design amplifiers with bandwidths that fit particular applications.

Equipment Used:

Power Supply

Oscilloscope

Function Generator

Breadboard

Jumper Wires

2N3904 NPN Transistors

10x Scope Probes

Various Resistors and Capacitors

Background:

Frequency Response of Amplifiers

Electrical engineers need to understand the intimate relationship between frequency and time. Circuits can be characterized both in time and frequency domain. It is important that an electrical engineer be able to travel between these two worlds effortlessly. Sometimes, a circuit problem that is difficult in one domain can be easily analyzed in the other domain. A good place to begin the study of the time-frequency relationship is in the design and analysis of a transistor amplifier circuit.

An amplifier can be characterized by many properties. The most obvious one that comes to mind is gain. One would certainly like to know how much their circuit amplifies. However, gain is not constant with frequency. If it was, then one could use their stereo amplifier to amplify any electrical signal regardless of frequency, obviously this would reduce the demand for electronics engineers. Luckily, the relationship between gain and frequency can be quite complicated and ensures the continued employment of electronics engineers. Generally an amplifier has a lower limit and an upper limit to the frequencies that it can amplify. These limits can have many names such as **lower -3dB point, upper -3dB point, Fl, Fh, lower corner frequency, upper corner frequency**, etc. It is best to refer to these limits as the lower and upper -3dB frequencies or corner frequencies.

These frequencies are determined by the time constants in the circuit. RC time constants are the most commonly found in electronics. The -3dB frequency is defined as

$$F_c = \frac{1}{2\pi RC}$$

The significance of this frequency is that the power of the circuit's output is halved compared to some reference point. Since voltage is usually the quantity of interest, when the voltage falls to 0.707 or $\frac{1}{\sqrt{2}}$ of the reference level at a particular frequency that is the corner frequency. To see the behavior of an RC time constant across frequencies, a transfer function is needed. A transfer function is the relationship between input and output amplitudes with frequency as a variable. Transfer functions can be quite complicated and the entire field of control theory is dedicated to their analysis. We will simply accept that the transfer functions for first order highpass and lowpass filters are as follows:

$$\text{Highpass: } \frac{V_{out}}{V_{in}} = \frac{j\omega RC}{j\omega RC + 1}$$

$$\text{Lowpass: } \frac{V_{out}}{V_{in}} = \frac{1}{j\omega RC + 1}$$

We can simulate these transfer functions in LTSpice. Fig. 1 shows the schematic of first order highpass and lowpass filters. Fig. 2 shows the amplitude and phase relationships for the two filters. The phase is shown by dashed lines and measured with the right axis.

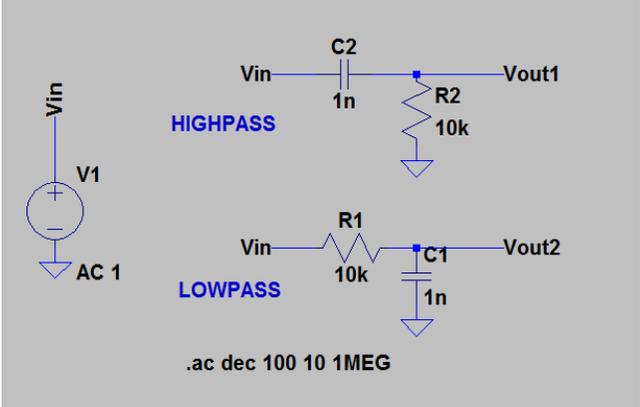


Fig. 1 1st order highpass and lowpass filters

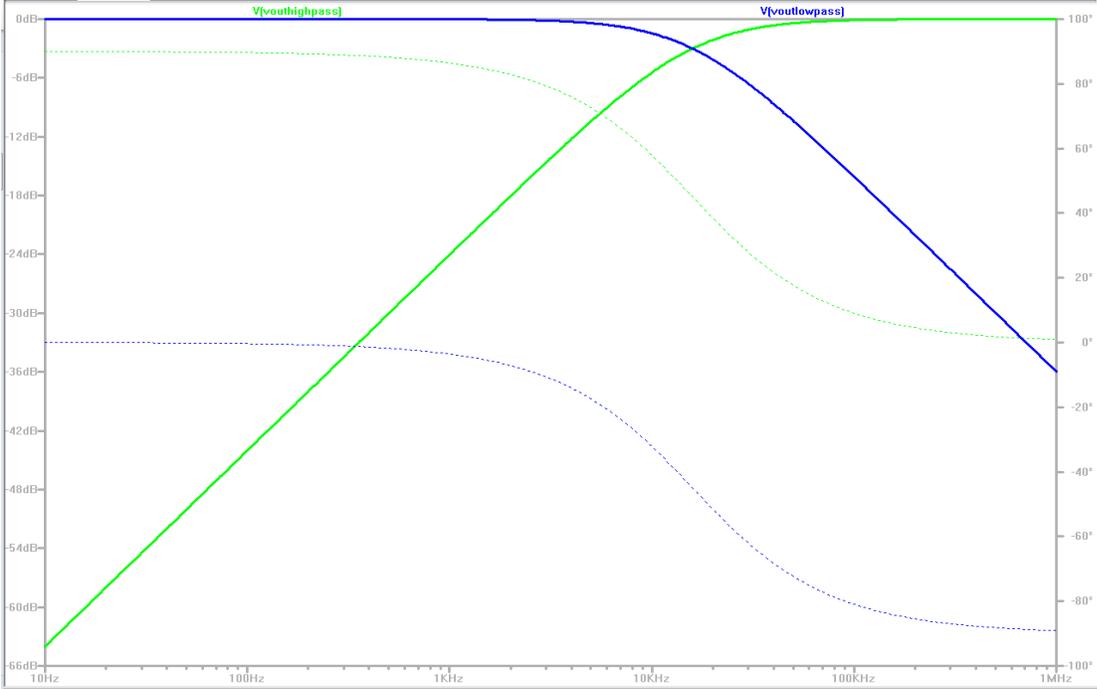


Fig. 2 Amplitude and phase of lowpass and highpass filter.

The important lesson here is that whenever a resistor and a capacitor appear together in a circuit we should expect some sort of frequency dependent behavior.

A typical amplifier displays frequency dependent behavior because of the various time constants in the circuit. Often the transfer function of an amplifier can be quite complicated to analyze so Spice is an essential tool. Consider the amplifier shown in fig. 3. We can see that there are three capacitors in the circuit and therefore at least three time constants. The transfer function could be quite difficult to derive by hand.

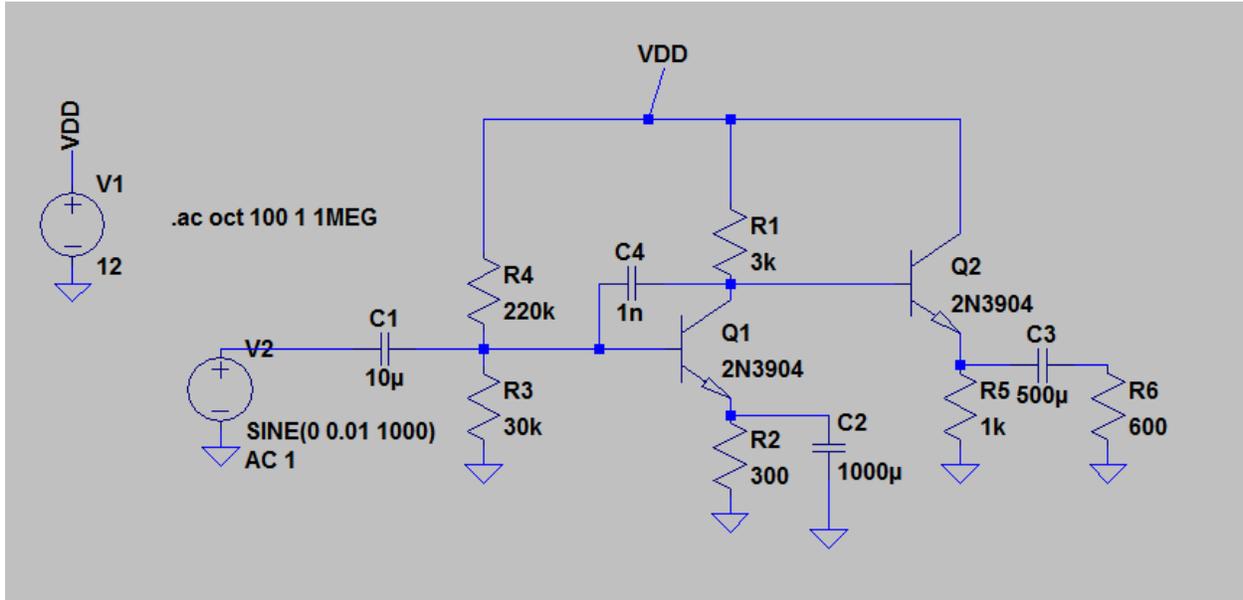


Fig. 3 Schematic of a simple two stage amplifier.

The frequency response of this amplifier can be seen in Fig. 4. Notice that the response is constant in the middle of the frequency range. This is referred to as the **midband gain**. Our design target gain for the amplifier is in this region. To the sides of the midband, the amplifier rolls off and the lower and upper corner frequencies are 14Hz and 58 KHz respectively. There are three time constants that control the lower corner frequency and these are formed by C1, C2 and C3 and their respective Thevenin equivalent resistances. Generally these time constants interact but for simplicity we will analyze each by itself.

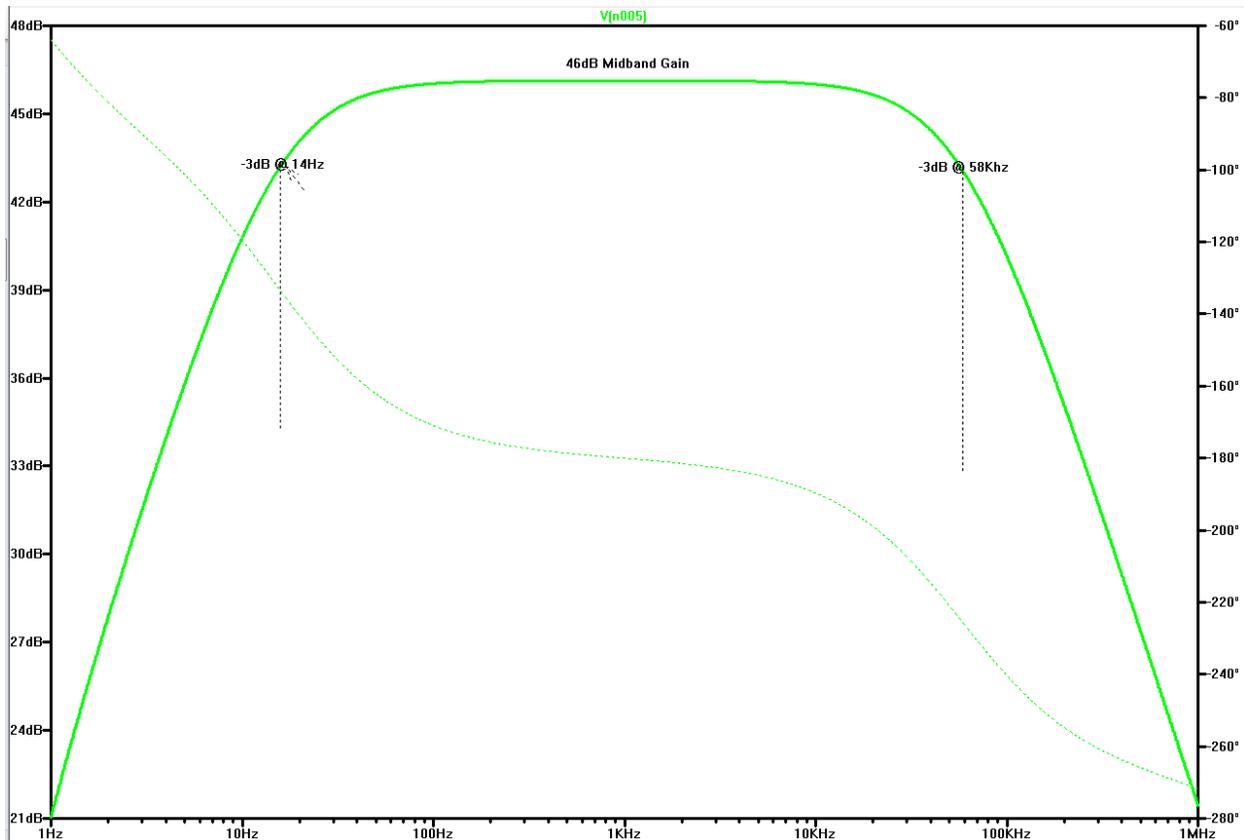


Fig. 4 Frequency response of amplifier with -3dB points labeled.

First we need to set up the Thevenin equivalent resistances. For C1, the resistances connected to it are R3 and R4 which are the biasing resistors, R_{π} which is the resistance of a transistor from base to emitter, the signal source's output resistance, and the reflected emitter resistance. The first network is shown in fig. 5. Recall that R_B is the parallel combination of the biasing resistors. It may be confusing to understand where the values of R_{π} and $R_{E_Reflected}$ come from. R_{π} is given by

$$R_{\pi} = \frac{V_T}{I_C} * (\beta + 1)$$

$R_{E_Reflected}$ is given by

$$R_{E_Reflected} = R_e * (\beta + 1)$$

This is an important result to remember. Resistances on the emitter side of a transistor affect the resistances on the base side of the transistor and vice versa. For example, if we have an emitter resistor of 300 ohms then the resistance seen from the base side is $300 * (\beta + 1)$. The implication for this is that we can control the input impedance of the transistor by setting the value of the emitter resistor.

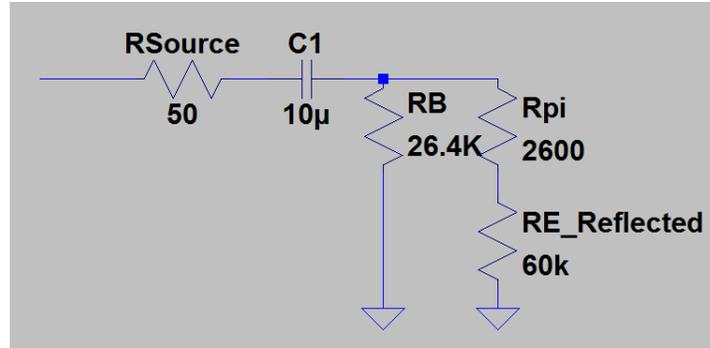


Fig. 5 Equivalent network seen at the transistor base.

Using basic circuit theory the resistances combine in series and parallel and the time constant of this circuit becomes

$$\tau = C1 * ((RB || (R\pi + RE_{Reflected})) + R_{Source})$$

Notice how Rpi and Rsource are relatively small so in the interest of simplicity we will ignore them in calculating the corner frequency although for an exact analysis they should be included. The corner frequency assuming a transistor beta of 200 is

$$F_c = \frac{1}{2\pi * (C1 * (RB || RE_{Reflected}))} = \frac{1}{2\pi * (10\mu F * (26.4k || 60k))} = \frac{1}{0.1833} = \mathbf{5.454Hz}$$

We can repeat this method to find all the corner frequencies in our circuit. In the interest of brevity we won't go through a detailed analysis of the equivalent circuits. The corner frequency for the network connected to the emitter of the transistor Q1 is given by

$$\begin{aligned} F_c &= \frac{1}{2\pi(C2 * ((Re' || Re) + \frac{RB}{\beta + 1}))} = \frac{1}{2\pi(C2 * ((\frac{V_T}{I_C} || Re) + \frac{RB}{\beta + 1}))} \\ &= \frac{1}{2\pi(10\mu F * ((13 || 300) + 132))} = \frac{1}{2\pi(1000\mu F * 144.46)} = \frac{1}{2\pi * 0.144} \\ &= \mathbf{1.1Hz} \end{aligned}$$

Finally the corner frequency for the network connected to the emitter of Q2 is given by

$$\begin{aligned} F_c &= \frac{1}{2\pi * (C3 * ((Re || Re' || Rload) + \frac{3k}{\beta + 1}))} = \frac{1}{2\pi * (500\mu F * ((1k || 5 || 600) + 15))} \\ &= \frac{1}{2\pi * (500\mu F * 19.93)} = \frac{1}{0.0628} = \mathbf{16Hz} \end{aligned}$$

There are a total of three time constants that determine the low frequency response of this circuit. How do we define our -3dB frequency? It should be obvious that the network with a corner frequency of 16Hz will be dominant. The other networks add to the roll-off as their corner frequencies are approached. This effect is shown in the graph of Fig. 6. The slope increases one order, that is, 20dB/decade each time a new corner frequency is encountered.

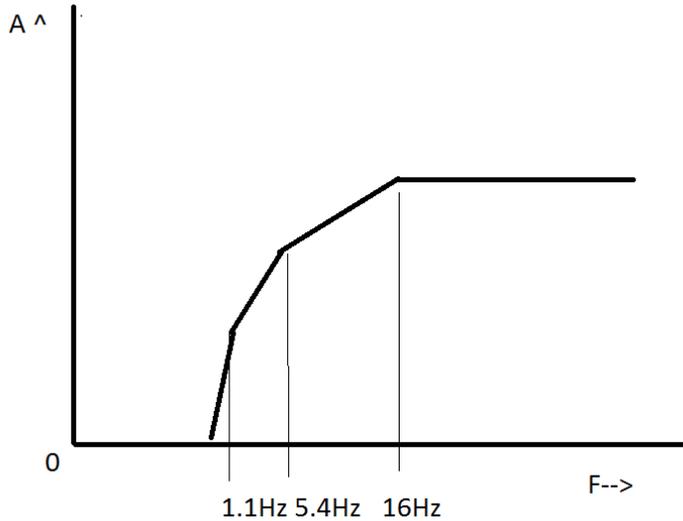


Fig. 6 Roll-off slope and frequency.

Next we look at the time constants that affect the high frequency response of the circuit. Generally, these time constants are the result of intrinsic capacitances within the transistor itself. Although usually it is desired for amplifiers to have as wide a bandwidth as possible, this can result in unwanted oscillations or RF interference. To prevent this, a capacitor can be connected between the base and collector of a transistor to introduce a high frequency roll-off. There is a caveat to this though. The capacitance connected between the base and collector has a much greater effect than its value would suggest. This is due to the **Miller Effect**. The miller effect is the multiplication of the capacitance connected between the input and output of an amplifier by the gain of the amplifier. This capacitance is then placed between the input and ground by use of **Miller's theorem**. The proof of this theorem is outside the scope of this lab. It can also be difficult to apply Miller's theorem properly.

$$C_{miller} = Gain * C_{BC}$$

If we are using a function generator with 50 ohm output impedance then a 1nF capacitor connected between base and collector with a gain of 100 will give us an upper corner frequency of:

$$F_{corner} = \frac{1}{2\pi * C_{miller} * R_{gen}} = \frac{1}{2\pi * 100nF * 50} = \mathbf{31.8Khz}$$

To keep things simple we won't examine the miller effect in the lab exercises but it is very important to always remember that the effect is there and is the main limitation on high frequency performance for many amplifiers. One should also note that the lowest possible **source resistance** (the output resistance of the previous stage) should be used if wide bandwidth is desired.

The Time-Frequency Relationship

A mathematician will likely explain the relationship between time and frequency through the use of Fourier transforms. While Fourier transforms are very useful and come into play in more advanced electrical engineering courses, they don't really help us in the lab. It is possible to empirically determine how a circuit's behavior changes with frequency. The main motivation for this in the lab setting is that instruments which can directly display results in frequency domain are usually very expensive. But luckily time domain instruments like the common oscilloscope can give us insight into the frequency domain behavior of a circuit.

The easiest way to measure the frequency response of an amplifier would be to connect a sweep function generator to the input and a spectrum analyzer to the output. This would instantly produce the frequency response. If one can't afford a spectrum analyzer they could vary the function generator themselves and note the amplitude of the output on an oscilloscope to create a frequency response plot. The disadvantages to this are tedium and possible limitations of the function generator. What if the amplifier's bandwidth exceeded that of the function generator? Luckily there is a better way to quickly test the frequency response of an amplifier.

This better method is square wave testing. The response of an amplifier to a square wave gives valuable insight into its frequency domain performance. Recall that an ideal square wave has an instant rise and fall time with an "on" time of any duration. Of course, the rise and fall times will have finite values but should be as short as possible. Fig. 7 shows how to translate square wave response to the frequency response. The rise time of the square wave at the output of the amplifier directly translates to the upper frequency limit of the amplifier. This relationship is described as:

$$Risetime \approx \frac{0.35}{F_c} \text{ or } F_c \approx \frac{0.35}{Risetime}$$

The low frequency testing is a bit more empirical. If the frequency of the square wave is near the lower frequency limits of the amplifier then the top of the square wave will be tilted with an exponential characteristic. This is due to the capacitors that set the lower frequency limit discharging significantly before the square wave changes. A good rule of thumb is, once any tilt appears, that frequency can conservatively be defined as the lower corner frequency. This behavior is shown in Fig. 8.

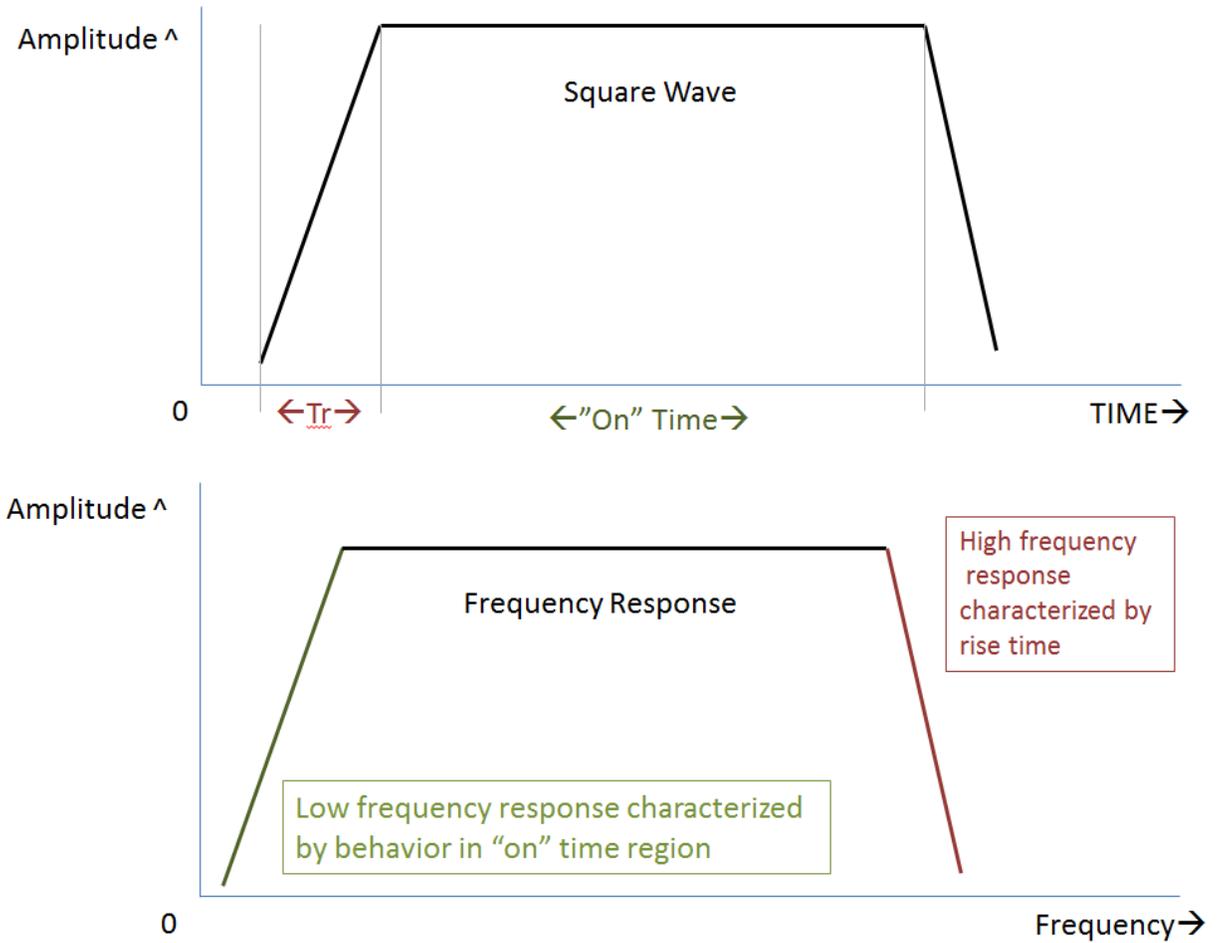


Fig. 7 Inferring frequency response from square wave response.

Finally, frequency aberrations within the pass-band can also be determined through square wave testing. Suppose that sinusoidal “ringing” is observed on the top of the output square wave. This implies a resonance centered at the frequency of ringing. This is shown in Fig. 9. In some cases very significant ringing can indicate a stability problem.

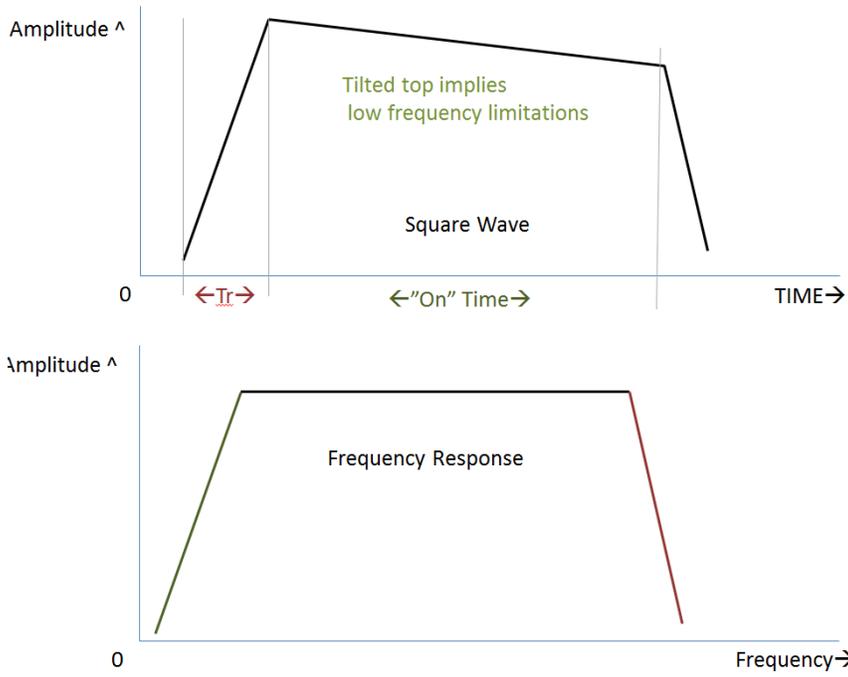


Fig. 8 Square wave and low frequency response

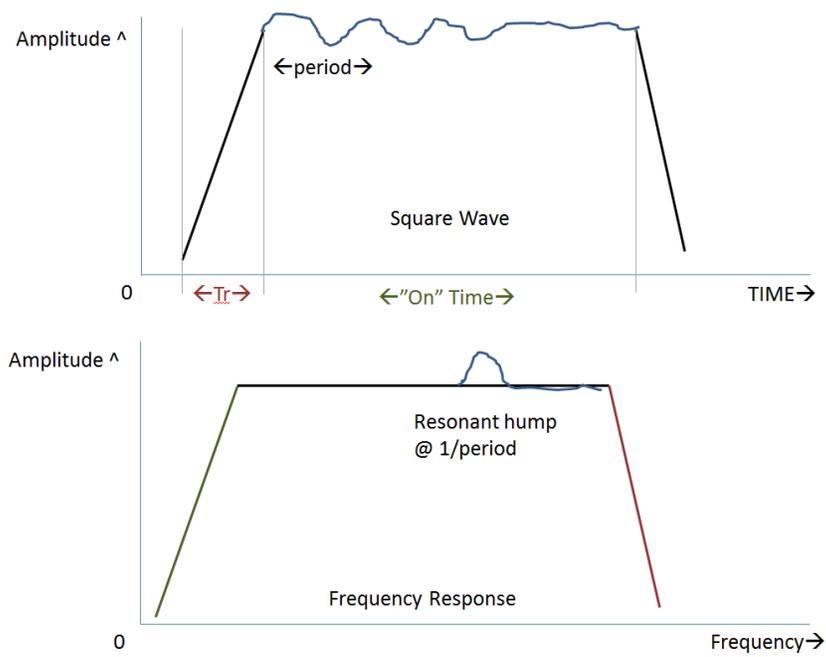


Fig. 9 Resonance

Prelab:

Analysis 1: Transient Analysis of Two Stage Amplifier

Draw the circuit in LTSpice as shown below.



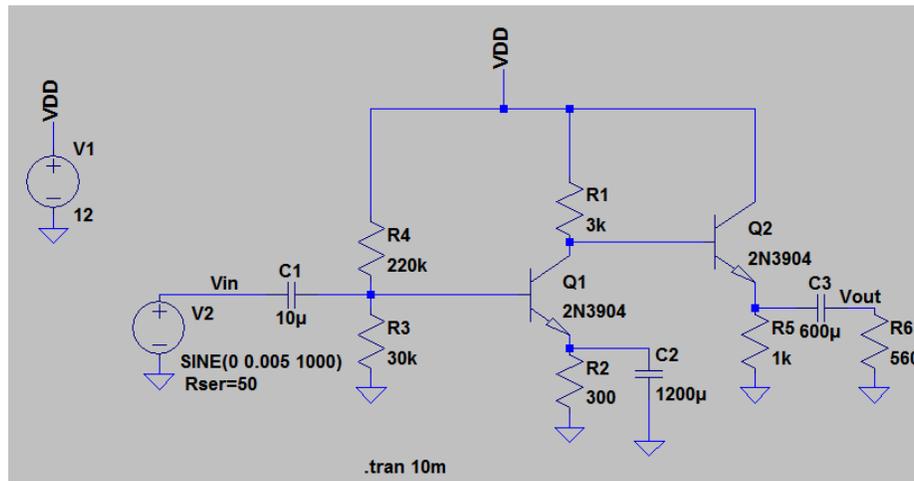


Fig. 10

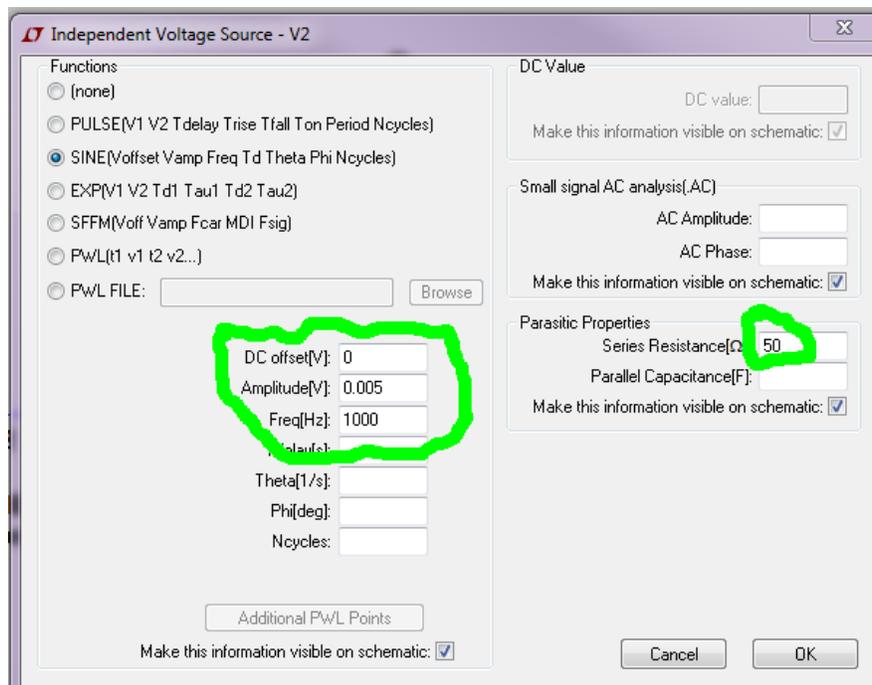
Right click on the input voltage source and the following dialog will come up. Enter the values as shown. The series resistance models the 50 ohm output impedance of our function generator.



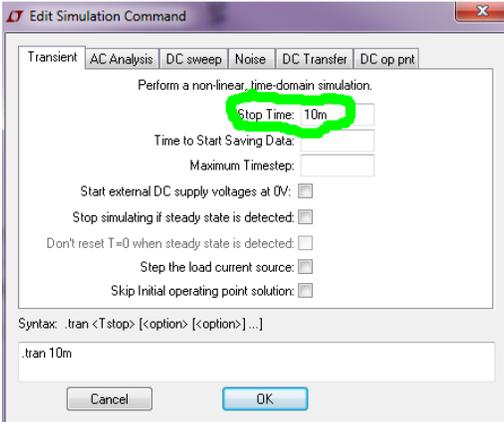Edit the simulation command and set the transient analysis to a stop time of 10m.




Probing the input and output and putting them on separate plot panes gives the graph below. Note the different amplitude scales. The output swings from roughly +/- 1V and the input is between +/-5mV.

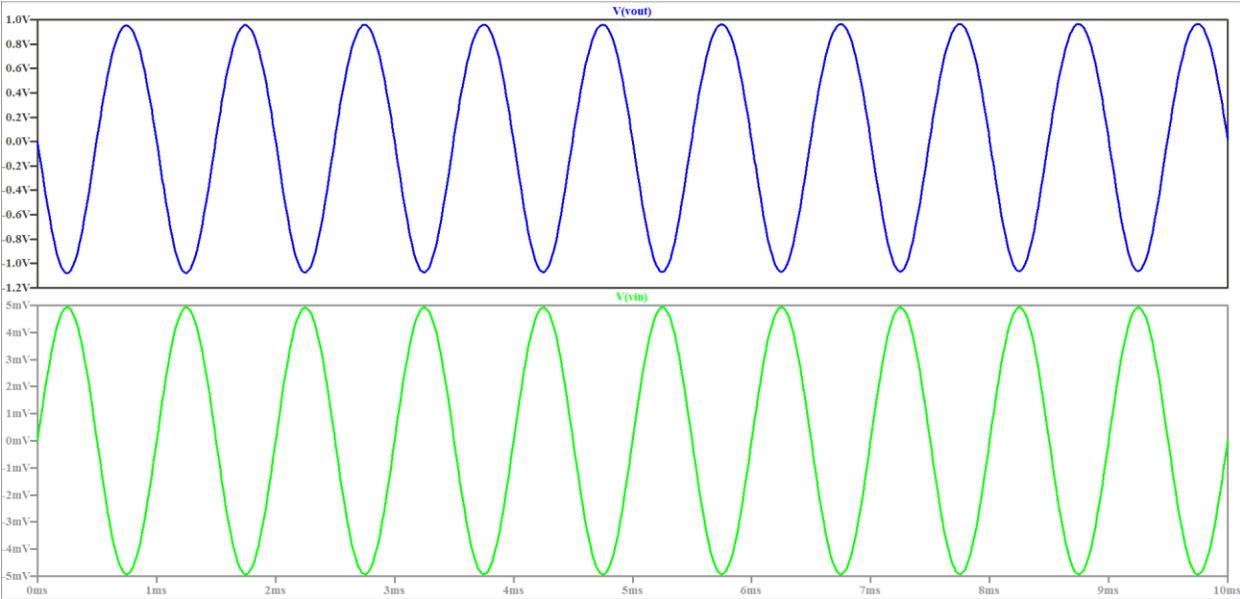


Analysis 2: Frequency Response of Two Stage Amplifier

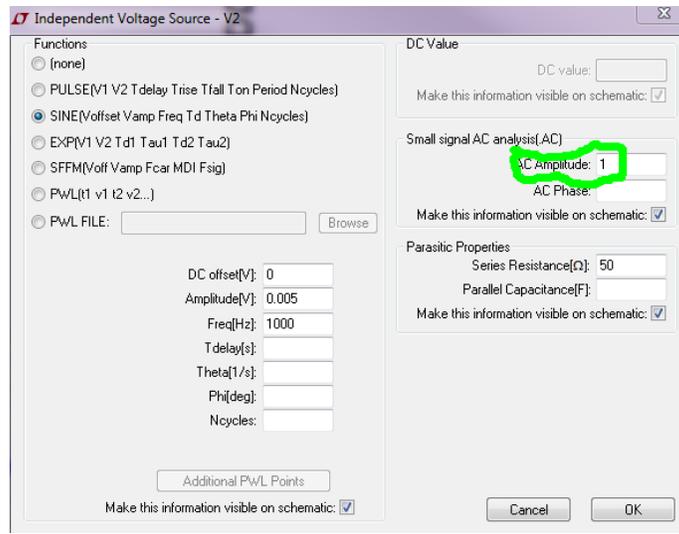
From the schematic in analysis 1, edit the input voltage source and enter a value of 1 in the “AC Amplitude” box as shown below. This sets a value of 1V for the AC source for small-signal analysis. This is convenient because 1V is referenced to 0dB in LTSpice. This does not imply at all that the amplifier will actually work with a 1V input.



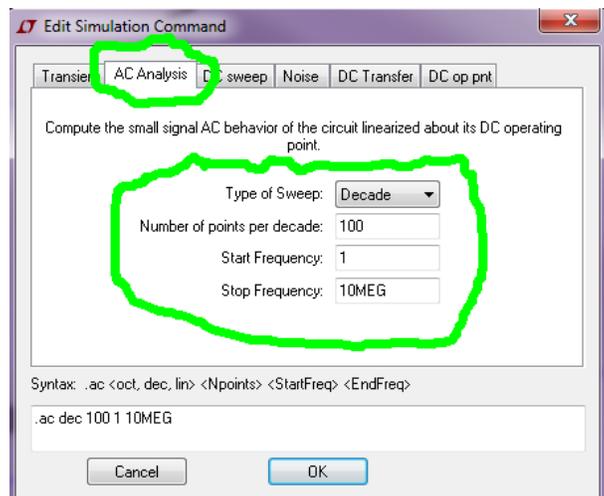Then edit the simulation command. In the AC Analysis tab select decade sweep, 100 points per decade, start frequency of 1 and stop frequency of 10MEG. The start frequency for AC analysis must always be 1 or greater.



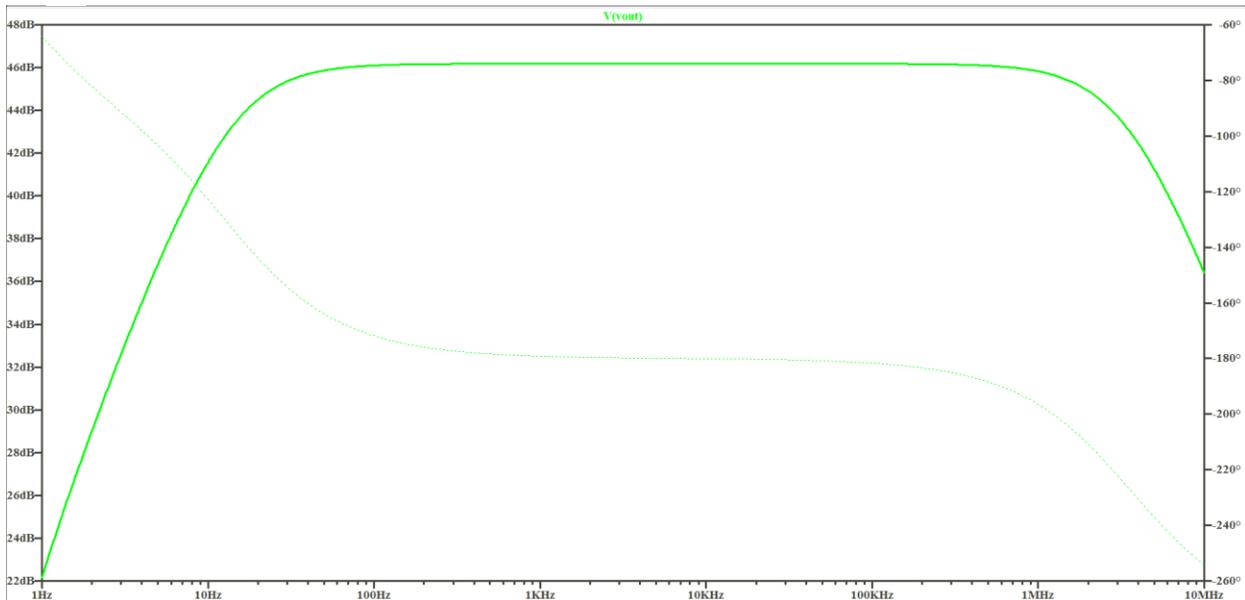Running the simulation and probing the output will show the following graph. Note the midband gain of around 46dB and the lower and upper corner frequencies of 13 Hz and 3.5 MHz respectively.



Prelab Deliverables:

- 1. Perform both analyses and submit screenshots of the schematic, transient response and frequency response.**
- 2. Email your .asc file to your instructor.**

Lab Experiments:

Experiment 1: Rise Time of Function Generator

We must first characterize our test equipment and verify we can use them for our lab. Directly connect the function generator to the oscilloscope. Ideally this should be done with a coaxial cable but if not available in the lab the crude scope probe to function generator probe method can be used. Set the function generator to 1V amplitude and 10 KHz square wave. Zoom in on the rising edge of the square wave and measure the time it takes for the output to rise from 10% to 90% of the final amplitude of the square wave. This is the rise time. Note this measurement. Some scopes will calculate this automatically for you, but a visual inspection is a good idea.

Experiment 2: Two Stage Transistor Amplifier

Circuit Description:


We will be constructing the circuit simulated in the prelab. Some background will help us understand the circuit. This circuit is a two stage amplifier consisting of a common emitter stage and an emitter follower (common collector stage). The load resistor approximates a 600 ohm load which is a common value for high quality headphones. It is also historically important impedance for telephone circuits just as 50 ohm loads are for RF. The emitter follower's emitter resistance is higher than the load resistance. This will limit the output voltage swing into the load because the circuit will be current limited by this resistor. This was done intentionally to illustrate that the output impedance of an emitter follower is not the emitter resistor. The performance of the amplifier can be improved by reducing the emitter resistor. The collector of Q1 is at 6V set by the biasing circuit. For the sake of completeness we will go through the biasing procedure followed to arrive at the bias circuit.

1. Decide on a collector current (2mA in this example).
2. Decide on what we want the collector voltage to be (6V in this example)
3. Pick a collector resistor based on the collector current and collector voltage ($6V/2mA=3k$).
4. Decide on a nominal DC gain ($Gain=Rc/Re$, gain chosen to be $10=3k/300$).
5. Estimate base current (assumed beta to be 200, $2mA/200=10uA$)
6. Calculate emitter voltage ($I_e*Re=2mA*300=0.6V$)
7. Add forward bias diode drop to emitter voltage to get base voltage ($V_{be}+0.6V=1.3V$)
8. Design voltage divider that sets base voltage to 1.3V and allows 5*base current to flow).


Experiment 2 Procedure:

1. Build circuit as simulated in the prelab.
2. Apply a 10mV 1 KHz signal to the input and look at the output of the amplifier on an oscilloscope. Note the amplitude of the output signal and calculate the gain of the amplifier. This will be our midband gain. Take a picture of the scope screen.
3. Begin reducing the frequency of the function generator until the output amplitude is 0.7 times the amplitude at 1 KHz. This is the lower 3dB frequency. Carefully measure this point (use cursors) in order to accurately compare to simulation results. Take a picture of the scope screen.
4. Increase the frequency of the function generator until the output amplitude is 0.7 times the amplitude at 1 KHz. This is the upper 3dB frequency. Carefully measure this point (use cursors) in order to accurately compare to simulation results. Take a picture of the scope screen.
5. Change the signal to a 1 KHz square wave. Zoom in on the rising edge of the square wave and measure the rise time. Take a picture of the scope screen. Notice any ringing in the square wave and if present try to find the period of the oscillation.
6. Begin reducing the frequency of the square wave until the square wave begins to droop. Take a picture of the scope screen.


Experiment 2 Example Pictures:

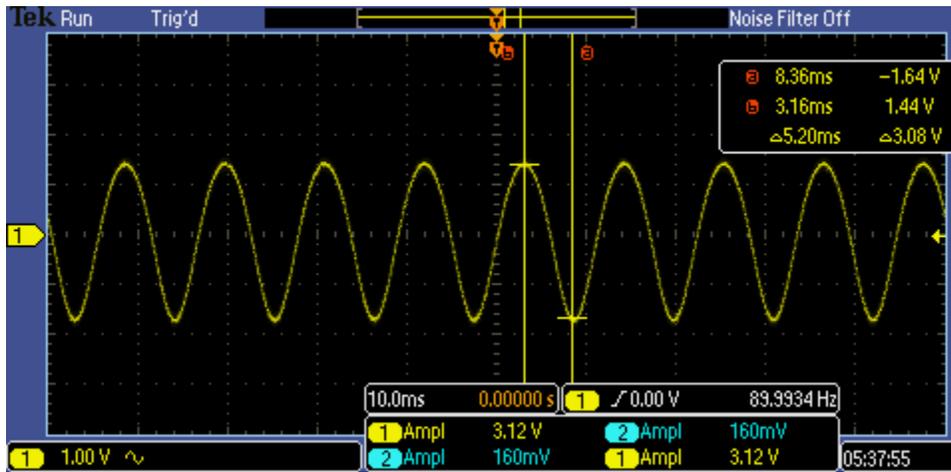


Midband Frequency

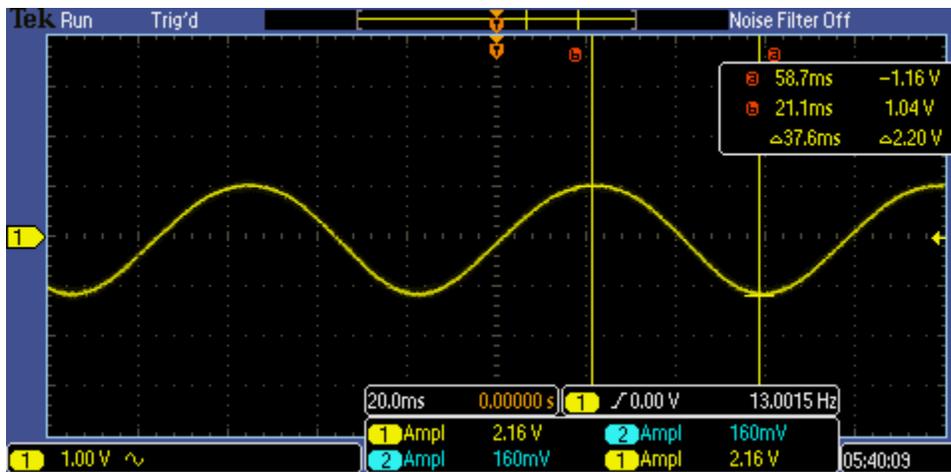


Lower Corner Frequency

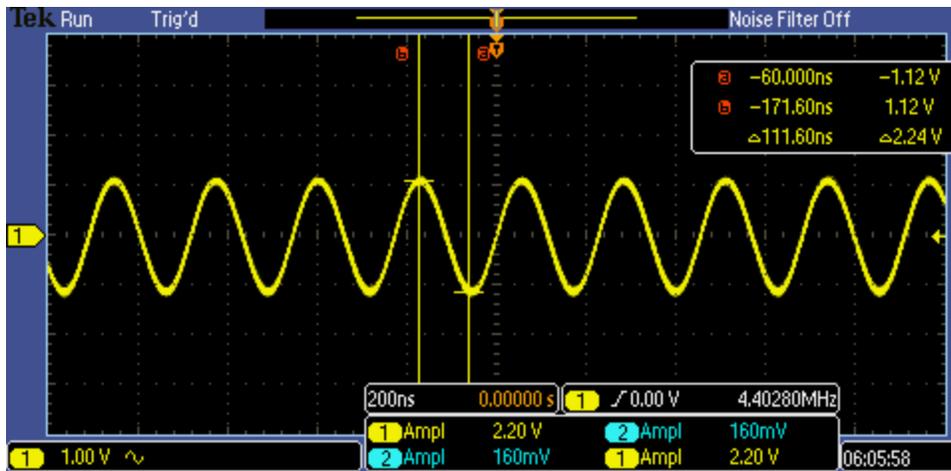


Upper Corner Frequency

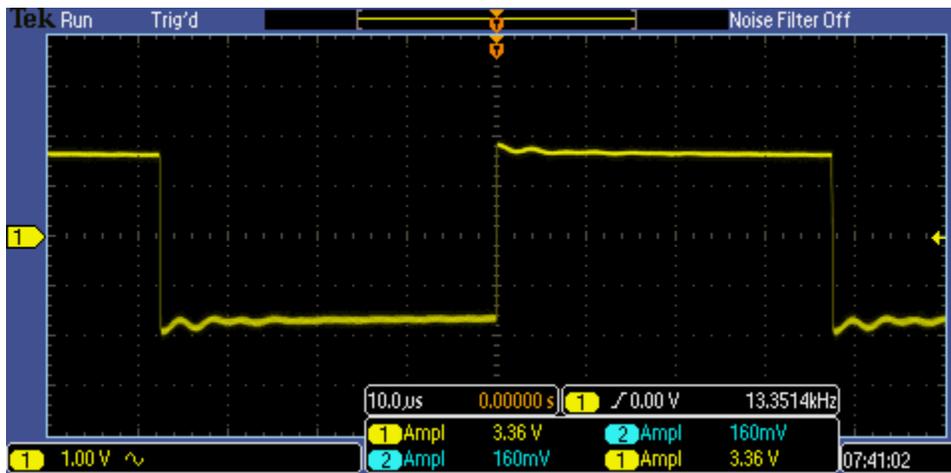

Output Square Wave

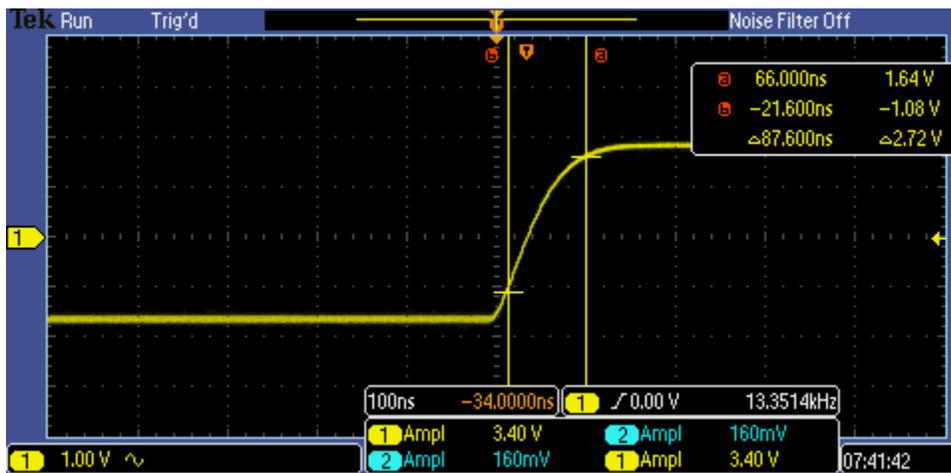

Rise Time Measurement

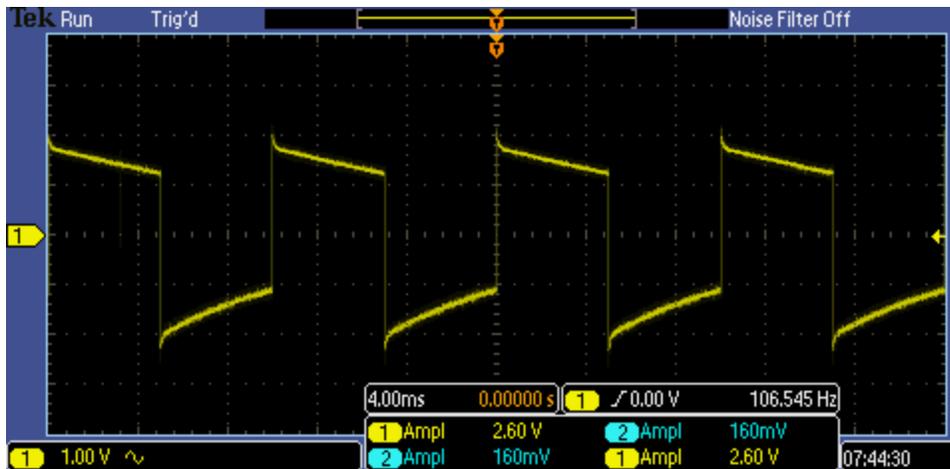

Droopy Square Wave.

Postlab Deliverables

1. All indicated scope screenshots.

Questions:

1. What was the midband gain of your circuit and how does this compare to your simulation results? Remember gain in dB is: $Gain\ dB = 20 * \log_{10}\left(\frac{V_{out}}{V_{in}}\right)$
2. What were your upper and lower corner frequencies? How do these compare to your simulation results?
3. Was there any ringing in your square wave response? If so what frequency was the ringing at?
4. Speculate as to why you had ringing in your measured results yet not in your simulations? (If you didn't have ringing, still speculate what could cause it.)
5. Based on your answers to 2 and 3 sketch a frequency response graph by hand.
6. Regarding results from experiment 1, does the measured rise time of the function generator affect the accuracy of our results?
7. Write a few sentences about the guy after whom the Miller effect is named.