

This two-band mobile s.s.b. transmitter is capable of up to 100 watts peak output, depending upon the power supply. Built on the chassis of a BC-458 transmitter, it uses the original VFO portion and the two output tubes. The phasing type of s.s.b. generation is used, and the audio amplifier has adequate gain for use with a crystal microphone.

On the panel, the upper knobs control output stage tuning and loading. The indicator light is used instead of a plate milliammeter, and the upper toggle switch is one of the two band switches. (The other bandswitch can be seen on the right-hand side of the chassis.) The lower left-hand knob is for the audio gain control, the toggle switch selects the sideband, and the two pointer knobs next to the switch are for carrier balance adjustments of the balanced modulator. The remaining knob tunes the VFO.

## Cheap and Easy S.S.B.

*Sideband Exciter Built Around the BC-458*

BY ANTHONY VITALE,\* W2EWL

• The following letter, quoted in its entirety, is self-explanatory.

Editor, *QST*:

Several months ago, Tony Vitale, W2EWL, was kind enough to give our radio club, the Ridgewood Amateur Radio Club, a talk on "Single Sideband."

Tony brought along a new exciter which he designed, built on a BC-458 chassis. It created a lot of interest among our members, with its compactness and very low building cost compared with the commercial exciters on the market. I was one of the many members bitten by the s.s.b. bug, and I have built this exciter. Several of our members have built them also, and they are very pleased with the results. Tony's talk was entitled "SSB Cheap and Easy," and it certainly turned out so.

My purpose in writing is to tell how pleased I am with this exciter. I have had many FB QSOs with it on very low power, and it didn't cost me over \$35, including the power supply. Most all of the fellows I talked with wanted to know more about this exciter, and I think it would be an excellent article to put in *QST*. We have named it the "W2EWL Special".

73,

Frank Hernandez, W2MOE

Glad to oblige, Frank; here is the "W2EWL Special".

**M**OST AMATEURS have either heard or actually experienced the advantages of single-sideband phone. The author's interests have been directed at mobile s.s.b. operation, because the boost in "talk power" for a given power supply one gets with s.s.b. really works to advantage in mobile work. W2EWL has been on 14-Mc. mobile s.s.b. for over 3 years, and during that time has participated in four-way QSOs involving ZLs and VKs, and a 7-way involving two African countries, one European country and three W call areas. The DX currently stands at WAC and 23 countries.

The exciter/transmitter to be described is not a one-of-a-kind deal, but represents a design that has evolved over the years. It is built around the VFO portion and on the modified chassis of a BC-458 (or T21/ARC-5), which tunes 5.3 to 7.0 Mc. in the original unit. These units sell from \$3.95 to \$7.95 in the surplus market, depending upon their condition. The design to be described uses the original output stage of the BC-458; the output will vary with the available plate voltage, and will be about 100 watts peak with a 1000-volt supply. The current W2EWL rig uses only one of the two 1625s in the original output stage, with 300 volts on the plate, to drive one 837 that in turn drives four 837s in a grounded-grid amplifier. The exciter hangs under the dash of the car, and the amplifier mounts in the trunk.

### *The Circuit*

The photographs show two different units; one is for 14 Mc. only and the other is switchable to either 14 or 3.9 Mc. If you want only 3.9- or 14-Mc. operation, you can omit the unwanted circuits and a couple of toggle switches, but the rest of the circuit remains unchanged.

\* East Glen Road, Denville, N. J.


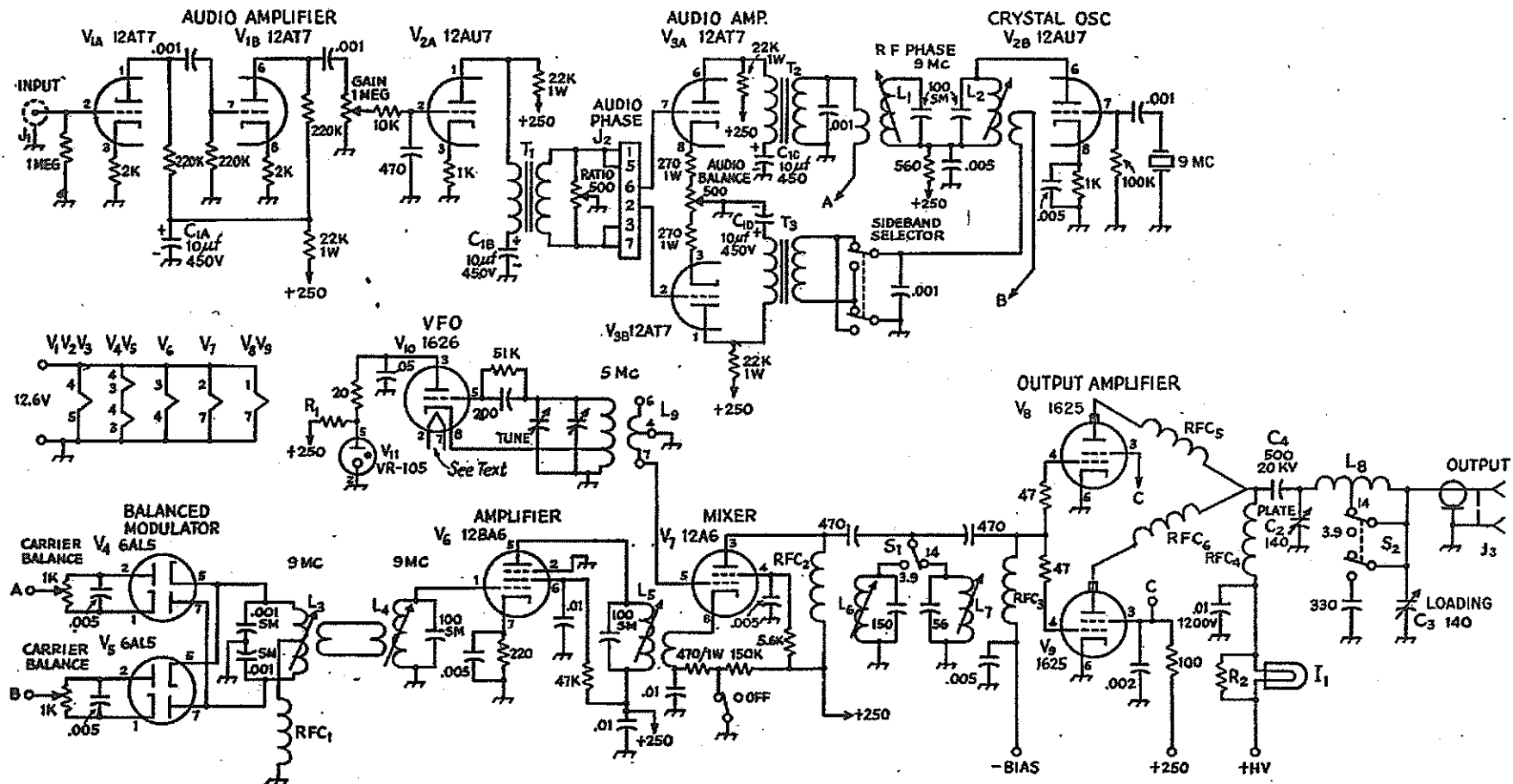


Fig. 1 — Schematic diagram of the mobile s.s.b. transmitter. Resistors are  $\frac{1}{2}$  watt unless otherwise noted. Decimal capacitance values are in  $\mu$ . SM = silver mica.

- C<sub>1</sub> — Quadruple electrolytic, 10-10-10-10  $\mu$ f. at 450 volts.  
 C<sub>2</sub>, C<sub>3</sub> — 140- $\mu$ f. midget variable (Hammarlund HF-140).  
 C<sub>4</sub> — 500- $\mu$ f. 20-kilovolt ceramic.  
 R<sub>1</sub>, R<sub>2</sub> — See text.  
 Coils L<sub>1</sub> through L<sub>7</sub> are wound on slug-tuned forms  $\frac{3}{16}$  inch in diameter. See text.  
 L<sub>1</sub>, L<sub>2</sub>, L<sub>4</sub>, L<sub>5</sub> — 25 turns No. 22 enam. Link, 4 turns

- hook-up wire.  
 L<sub>3</sub> — 8 turns No. 16 enam. 1-turn link.  
 L<sub>6</sub> — 40 turns No. 26 enam.  
 L<sub>7</sub> — 25 turns No. 22 enam.  
 L<sub>8</sub> — 46 turns No. 20 bare, wound 16 turns per inch, 1-inch diam. Tap at  $8\frac{1}{2}$  turns from C<sub>2</sub> end. (B & W 3015). For 14 Mc. only, use 12 turns No. 14 wound to occupy  $1\frac{1}{8}$  inches,  $1\frac{1}{8}$  diam.  
 J<sub>1</sub> — Microphone jack.

- J<sub>2</sub> — Octal socket.  
 J<sub>3</sub> — Small coaxial cable receptacle, UG-290/U.  
 RFC<sub>1</sub>, RFC<sub>2</sub>, RFC<sub>3</sub> — 500  $\mu$ h.  
 RFC<sub>4</sub> — 1 or 2.5 mh. 300 ma.  
 RFC<sub>5</sub>, RFC<sub>6</sub> — 20 turns No. 22 enam., wound on  $\frac{3}{16}$  inch form (high-value resistor) and spaced to occupy  $\frac{1}{8}$ -inch winding length.  
 T<sub>1</sub> — 20,000 to 600-ohm transformer. See text.  
 T<sub>2</sub>, T<sub>3</sub> — 20,000 to 200-ohm transformer. See text.

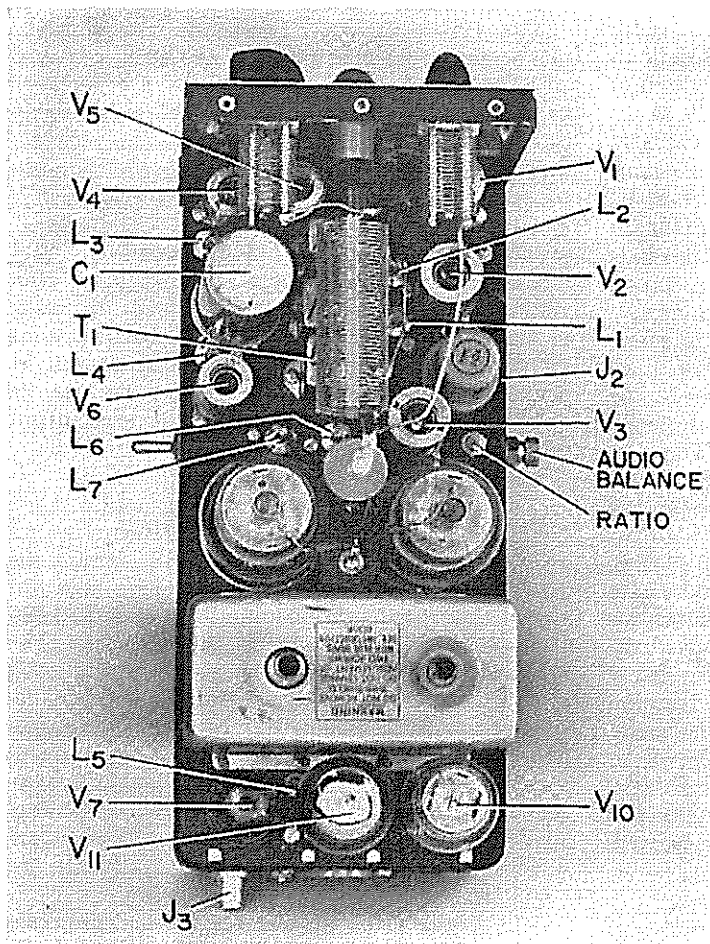

Top view of the two-band exciter. The B & W Phase-Shift network is in the light-colored "tube" plugged in  $J_2$ .

and a UG-290/U receptacle is added ( $J_3$ ). The socket for the 9-Mc. crystal can be mounted on a small bracket on the side of the chassis, under the  $V_2$  socket.

#### Oscillator Wiring

The numbers shown on  $L_9$  in Fig. 1 represent the numerical order of the terminals from the VFO assembly, reading from the rear to the front. The wire from Terminal 1 will have been removed, and the wires from 2 and 3 will be left as is. The black wire from 4 should be grounded to the chassis. The white wire from Terminal 5 ("hot" heater lead) is left connected to the .006- $\mu$ f. fixed capacitor and the "hot" side of

the 12.6-volt heater circuit. The black lead from 6 to the neutralizing capacitor is removed, and the lead from 7 is carried over to Pin 5 of the  $V_8$  socket.

On the oscillator socket,  $V_{10}$ , the red lead at Pin 3 that ran to the tuning-eye socket is removed, and the red lead from Pin 4 is run to Pin 5 of the  $V_{11}$  socket (old crystal socket). This is the pin to which  $R_1$  is connected; the value of  $R_1$  will be 5000 ohms, 5 watts, if a 250-volt supply is used.

#### Other Wiring

Not much need be said about the rest of the wiring, since everyone has his own pet tricks. In the construction of the coils  $L_1$  through  $L_5$ , the link windings are wound over the "cold" ends (grounded end) with the same wire that is used for the twisted link lines.<sup>3</sup> The single exception is the 1-turn link winding of  $L_3$ , and this winding should be dead center on  $L_3$ .

#### Adjustment

As in any transmitter, the initial adjustment is a step-by-step process. To do a good job with this unit, you should have an audio oscillator and a simple oscilloscope, which you may be able to borrow for the occasion if you don't have them in your shack. You will also need a receiver and, if you run into any troubles, a v.t.v.m. or other test meter.

(Continued on page 110)

for sockets, transformers, coils and potentiometers. Although larger transformers can be crowded into the available space, the small transformers shown in the photographs are very convenient.<sup>2</sup> Holes are also required for the insulator that supports  $C_4$ , for the mounting of  $RFC_4$ , and for the four-section electrolytic capacitor,  $C_1$ .


A new panel of sheet aluminum is used over the old panel. The tuning capacitors  $C_2$  and  $C_3$ , the pilot lamp  $I_1$  and the band-change toggle  $S_2$  are mounted on this panel above the level of the chassis deck. On the same panel, below the level of the deck, you will need holes for the two carrier balance potentiometers, the gain control, the microphone jack  $J_1$ ; the sideband selector switch (toggle) and the VFO tuning.

The ratio potentiometer is mounted on the left-hand side of the chassis (viewed from the front), and the audio-balance potentiometer is mounted on the deck near  $V_3$  and the audio phase-shift network. A CTC "Minipot" ( $\frac{3}{4}$ -inch diameter) will fit more conveniently here than the standard controls.  $S_1$  is mounted on the right-hand side of the chassis.

At the rear of the chassis, a regular octal socket can be substituted for the original power socket,

<sup>2</sup> The three transformers are available as a set from Electronics Associated, P.O. Box 206, Montclair, N. J. The price is \$7.95.
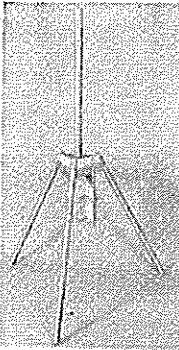
<sup>3</sup> We used coil forms from a surplus unit marked "Z101." The unit, with 12 of the coil forms in it, was obtained for \$1.50 from Vet Salco, Paterson, N. J.



**MAKE USE  
OF  
FULL  
TRANSMITTER  
POWER!**

with Western Gear's

**DELTA-TENNA**

1. Reduces standing wave ratio to minimum; helps minimize TVI problems; matches RG8U 52 ohm coax without resorting to any impedance matching device.
2. Extra large elements for uniformly excellent loading over the entire band.
3. Attractive gold anodized elements assure extra long life in any climate.
4. Occupies a minimum of space; low wind loading, light weight.
5. Built-in coax fitting; U bolts for installation to any type vertical support.
6. Meets or exceeds all FCDA requirements for Civil Defense use.
7. Models for all ham or commercial frequencies from 25 to 465 mcs.

**PRICES:** 2-meter—\$19.95, 6-meter—\$24.95,  
10-11 meter—\$29.95, 220 megacycles—\$18.95,  
432 megacycles—\$16.95

Order now through  
your distributor or:

**WESTERN GEAR CORPORATION**

Electro Products Division

132 W. Colorado St., Pasadena 1, Calif.

5592

Phone RYan 1-6604

(A few distributorships still available)

VE2DR 180, LM 71, EC 50, CP 37, GL 32, ATQ 18, FL 16,  
ALBERTA — SCM, Sydney T. Jones, VE6MJ — PAM,  
OD, RM: XG. The new officers of the Calgary Amateur  
Radio Club are HY, pres.; XB, vice-pres.; QS, treas.; WL,  
net. mgr. PV reports that the Lethbridge gang is having  
trouble with "ITV." EA, KF, AS, WO, and MJ are pro-  
gressing with 14.4-Mc. equipment. JP is working on a mobile  
rig. SS has overcome the difficulties in the rig and is heard  
regularly on 3.8-Mc. phone. KX is building a heterodyne  
exciter. HM upheld his usual standard in the November  
Frequency Measuring Test. YE and CE are heard checking  
the B.C. Net regularly. NX is the new EC for Edmonton.  
KL has qualified for phone operation. UK is on the lookout  
for a 3765-ke. crystal. Traffic: VE6HM 321, OD 78, YE 46,  
PS 10, VE7HD 10, VE6MJ 5, WL 3.

BRITISH COLUMBIA — SCM, Peter M. McIntyre,  
VE7JT — SEC: DH. Your SEC, Wm. Emerson, VE7DH,  
of Nanaimo, would welcome applications from ARRL  
members for EC appointments. With only a minimum of  
your time being involved and with just a little interest, he  
could have active ECs in all parts of British Columbia.  
Hope some of you heeded ASR's request to join RN7 and  
put British Columbia on the map again. Incidentally, ASR  
is the new Route Manager for B.C. The boys in Dawson  
Creek acquired new mobile emergency equipment for the  
club and still have money in the treasury. Most of the  
activity from Nanaimo seems to be on 2 meters with every-  
one building gear and antennas, even to GR's receiver that  
has no noise. Locally AQW has acquired a car, so needless  
to say there will be a new mobile on soon. AFP is moving  
his QTH to Victoria and ZF, ZV, and HC are going East.  
We wish them all well in their new ventures. Now is the time  
to get all the stuff ready for all the new antennas as spring  
is close at hand and the rigors of winter weather have taken  
their toll. Yours truly would like to thank the BCARA for  
the honor bestowed on me in giving me the BCARA Cup  
Award for this year. Traffic: VE7ASR 216, CQ 128, ACS  
80, AUF 53, XY 50, ZV 45, JT 31, AIO 24, DH 14, FS 14,  
AG 8, ABI 4.

SASKATCHEWAN — SCM, Harold R. Horn, VE5HR  
— BZ has changed his OBS frequency and is now heard on  
3795 kc. at 1815 hours Tue., Thurs., and Sat. WW has a new  
ground plane and works out well with it and a new TBS-50.  
LT is now all-band phone and uses voice-controlled carrier.  
JO is now at Kerrobert. BD has a new Viking Ranger and  
works 21-Mc. mostly. JA now is on phone and does well  
with 20 watts. BV and GX were heard talking over the  
best fishing spots and making plans for the coming season.  
BI puts out a nice signal with a DX-100 after being silent  
for a few years. LT and WW are new phone net members  
on 3780 kc. OC has a modified cubical quad for 14 Mc. The  
Saskatoon Club officers are BD, pres.; TH, vice-pres.; and  
DU, secy. Moose Jaw officers are WM, pres.; WA, vice-  
pres.; AV, secy.; and KG, treas. VL has a new 20-meter  
beam up 70 feet. Has your appointment been sent in for  
endorsement? If not, please do so right away. Traffic:  
VE5CW 39, BZ 32, LM 32, RE 30, CI 18, VL 16, DS 15,  
QL 12, GX 5, HR 5, DD 4, LJ 4, BF 2, BI 2, EQ 2, GO 2,  
LT 2.

**Easy S.S.B.**

(Continued from page 20)

When the wiring has been completed and you have determined that the tube heaters light up when 12.6 volts has been applied, remove  $V_5$  and  $V_9$  from their sockets and connect the 250-volt source. Check the oscillation of the VFO by listening on the receiver tuned to 5.3 Mc. If a 9.1-Mc. crystal is to be used, the VFO must tune 5.1 to 5.3 Mc. to cover 3.8 to 4.0 Mc. and 14.2 to 14.4 Mc. The tuning range of the VFO can be shifted with the trimmer capacitor and the tuning slug. If the transmitter is to be built for one-band operation, a crystal frequency can be selected that will require no modification of the BC-458 range.

With the VFO working, plug in the crystal and check for oscillation by listening on the receiver. Some adjustment of the slug in  $L_2$  may be required before the stage oscillates.

Next feed in a 1200-cycle signal at the microphone jack, using a very low-level signal. Peak  
(Continued on page 112)

# Are you fond of . . . .



## tinkering?

If you're the kind of guy that can't keep his soldering iron out of any radio gear—including a thousand-buck receiver—then QST is for you. Fresh ideas for major components, gadgets and test equipment, for VHF, SSB, a.m. and c.w., for antennas, couplers, keyers, monitors, and modulators—all show up regularly in QST.

But even if you've never built a thing, you'll want QST, for it also has the latest word in regulatory matters, contests, station activities, DX, emergency work, and of course, advertisements about the hottest commercial gear on the market from the most reliable sources.

If you're not now getting QST delivered to your door, sign up for your League membership and QST subscription today. Together, they cost just \$4 in the U. S., \$4.25 in Canada, and \$5 elsewhere.

**THE AMERICAN  
RADIO RELAY LEAGUE  
WEST HARTFORD 7, CONNECTICUT**

$L_3$ ,  $L_4$  and  $L_5$  for maximum signal. This can be checked with a small pick-up loop connected to the receiver through a length of shielded wire. The tuning of  $L_6$  and  $L_7$  and the output amplifier tuning controls can now be checked after the high-voltage supply is connected and the 1625s are plugged in. The correct operating bias must also be added, and it is hardly necessary to point out that the tubes should be plugged in while the power supplies are turned off, if you want to get on with your s.s.b. career. A 60-watt lamp can be used for a dummy load during initial tests, and the pick-up loop for the receiver can be placed near the lamp.

Now turn off the audio signal and adjust the two carrier-balance potentiometers for minimum output.

Next turn on the audio and adjust the ratio and audio-balance controls for minimum ripple on the scope pattern. If you aren't familiar with these "ripple" patterns and the correct way to couple a 'scope for r.f., the information is in the *Handbook*. It will undoubtedly be necessary to adjust  $L_1$  before the ripple can be reduced to a small value, and you will find that you have to go through these adjustments several times before you can get the ripple down. Be sure to keep the audio at a low level so as not to saturate a stage somewhere along the line. The initial sideband alignment checks are best made at 9 Mc., using the output of  $V_6$  link-coupled to a 9-Mc. tuned circuit connected to the vertical plates of the oscilloscope.

Check each sideband position, because in an ideal exciter they should both give the same minimum-ripple pattern. If you have an r.f. probe for your v.t.v.m., you can measure the r.f. voltages at the arms of the carrier balance controls and try to get the values within 10 or 15 per cent of each other. This is done by the tuning of  $L_1$  and  $L_2$  which will, of course, require further monitoring on the 'scope for minimum ripple.


Your objective is to minimize the ripple on the 'scope pattern and to have it similar for either position of the sideband selector switch. Once that has been done, you can connect the microphone and, whenever you need a single tone for tuning  $C_2$  and  $C_3$ , you can unbalance one of the carrier balance controls temporarily. If you want to run two-tone test patterns for checking the output-amplifier performance, remove  $V_4$  or  $V_5$  from its socket and use a low-level audio tone into  $J_1$ . The two-tone test procedure is outlined in the *Handbook* and the s.s.b. book.<sup>4</sup>

The 1625 bias will depend upon the plate and screen voltage. A fair rule of thumb is to adjust the bias so that the idling plate current (no signal) for the two tubes gives around 35 to 40 watts input for the two tubes. With 750 volts on the plates and 250 on the screens, you can start at a bias of  $-30$  and work down. With higher plate and screen voltages, it will be necessary to start proportionately higher.

(Continued on page 114)

<sup>4</sup> *Single Sideband for the Radio Amateur*, published by the A.R.R.L.

## DX-MINDED?

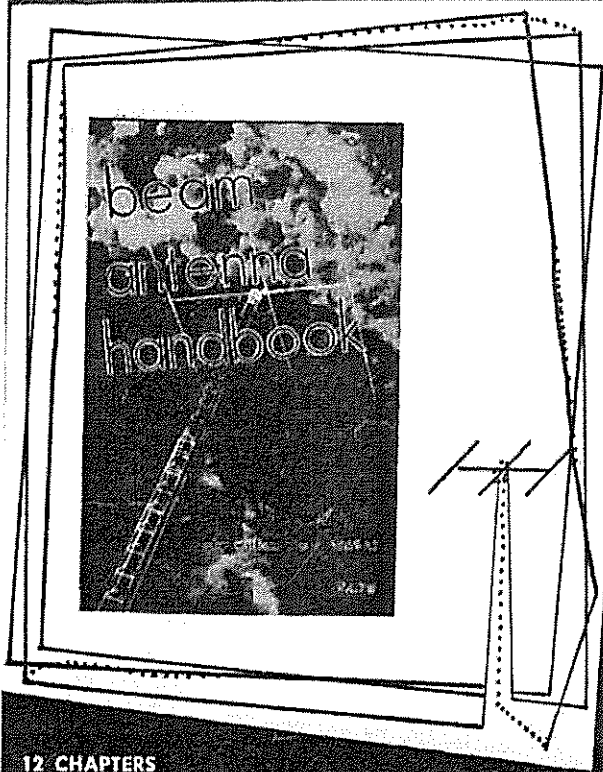

12 CHAPTERS  
\$2.70

## BEAM ANTENNA HANDBOOK

by William I. Orr, W6SAI

The first complete text entirely devoted to construction, installation and evaluation of rotary beam antennas. Eliminate "guesswork" in antenna construction and adjustment. New matching systems. Dimensional charts for beam design for 6, 10, 11, 15, 20 and 40 meter bands.

RADIO PUBLICATIONS INC.  
DANBURY RD., WILTON, CONN.

Please rush \_\_\_\_\_ copies of BEAM ANTENNA HANDBOOK at \$2.70 per copy to:

Name \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Enclosed:  check  cash  m.o.

### Mobile Operation

While the unit is an excellent one for home-station use and "getting your feet wet" in s.s.b., it was designed for mobile operation. The most common question you run into about mobile operation is "What do you use for a receiver," and "Isn't it hard to tune in s.s.b. in motion?" The answer to the first question is "Use a crystal-controlled converter into a BC-453 (190 to 550 kc.)." The answer to the second question is "No, not with a good tuning rate in the receiver," (which the converter/BC-453 combination has).

Voice-controlled break-in? Who needs it in mobile work? The push-to-talk switch is plenty good enough.

### 6.3-Volt Operation

The tubes specified in the schematic are for 12-volt heater operation, and the unit has been operated in a car with a 12-volt battery. For 6-volt mobile operation, it is suggested that one or two 6146s be substituted for the two 1625 output tubes. The other parts of the circuit remain the same, except that the heater wiring must be revised. A 6BA6 would be used at  $V_6$  and a 6V6 at  $V_7$ .

The author expresses his gratitude to Willie Sayer, W2NYY, and Dick Johnson, W2BDL, for their help in compiling information for this article.

## Multiband Phone

(Continued from page 38)

### Adjustment

The bands can be centered on the VFO dial by varying  $L_1$  for the two lowest-frequency ranges, and by varying  $C_2$  on the other ranges. If both ends of any band cannot be covered,  $C_2$  (or  $C_3$ ) must be decreased, and  $L_1$  increased slightly. On the other hand, if a band is not spread out enough over the dial,  $C_2$  (or  $C_3$ ) must be increased  $L_1$  decreased.

It should be possible to obtain at least 5 ma. of amplifier grid current on all bands. If the grid current exceeds this value, it can be reduced by detuning the 6AG7 output circuit. Although the 5894 has a rating of 150 ma. at 450 volts for 'phone operation, this is a CCS rating. The ICAS ratings of the Philips QQE06/40 are 600 volts, 180 ma. It is assumed that the 5894 or AX9903 could be safely operated at these ratings in amateur service.

The modulator tube is operated with 250 volts on the screen and 27.5 volts of bias. Idling plate current is 40 ma. rising to 125 ma. on peaks.

In TV areas, the customary practice of using shielded power wiring, power-lead filtering and a shielding enclosure should be followed as described in the ARRL Handbook.

— Ed