

Hemet High School
Automotive Technology

Name _____ Date _____ Period _____

Help Trace the Wiring Diagram Route

(Do the Maze in pencil, so you can erase wrong turns)

